

CONTENTS

<i>Preface to Third Edition</i>	(v)
<i>Preface to Second Edition</i>	(vii)

CHAPTER 1

Network Variables and Elements

1.1	Introduction	1
1.2	Network Model	1
1.3	Network Variables	2
1.4	Network Elements	6
	1.4.1 Active elements	6
	1.4.2 Passive elements	9
1.5	The Resistor	10
1.6	The Inductor	13
	1.6.1 Faraday's law of electromagnetic induction	13
	1.6.2 Self inductance	14
	1.6.3 Mutual inductance	19
	1.6.4 Dot convention	20
	1.6.5 Energy consideration in the magnetically coupled coils	22
1.7	The Capacitor	26
	<i>Problems</i>	32

CHAPTER 2

Kirchhoff's Laws and Resistive Networks

2.1	Introduction	37
2.2	Kirchhoff's Laws	38
	2.2.1 Kirchhoff's current law	38
	2.2.2 Kirchhoff's voltage law	39

2.3	Resistive Networks	40
2.3.1	Resistors in series	41
2.3.2	Resistors in parallel	44
2.3.3	The voltage divider	46
2.3.4	The current divider	47
2.3.5	Ladder network	49
2.3.6	Source transformations	51
2.3.7	Voltage source with no series resistance	52
2.3.8	Current source with no parallel resistor	53
2.3.9	Voltage sources with parallel resistors or current sources	54
2.3.10	Current sources in series with resistors or voltage sources	55
2.3.11	Star – delta or Y – Δ transformation	60
2.4	Node Voltage Method	66
2.5	Mesh Current Method	75
2.5.1	Dummy mesh current method	79
2.6	Magnetic Circuits	84
2.6.1	Magnetic fields	84
2.6.2	Some definitions	85
2.7	Properties of Magnetic Materials	86
2.7.1	B-H curves	86
2.7.2	Classes of magnetic materials	87
2.8	Simple Magnetic Circuits	87
2.8.1	Leakage flux and leakage coefficient	88
2.8.2	Composite magnetic circuits	89
	<i>Problems</i>	92

CHAPTER 3

Single Phase Circuits

3.1	Introduction	101
3.2	Characteristics of Periodic Functions	101
3.3	Average Value, R.M.S Value, form Factor	103
3.3.1	Average value	104
3.3.2	Effective value or RMS value	104
3.3.3	Form factor	107

3.4	Representation of a Sine Function	108
3.4.1	Trigonometric representation	108
3.4.2	Phasor representation	109
3.4.3	Complex algebra representation	110
3.5	Steady State Response of R, L and C Elements to Sinusoidal Excitations	113
3.5.1	Response of pure resistance	113
3.5.2	Response of pure inductance	116
3.5.3	Response of a pure capacitor	119
3.5.4	Series R – L circuit	123
3.5.5	Series RC circuit	128
3.5.6	Series RLC circuit	130
3.5.7	Parallel RL circuit	132
3.5.8	Parallel R C circuit	133
3.6	Series Resonance	141
3.6.1	Characteristics of a series resonant circuit	141
3.6.2	Q – factor	145
3.6.3	Selectivity and bandwidth	147
3.6.4	Voltage across the capacitor	149
3.6.5	Voltage across the inductor	150
3.6.6	Resonance by varying capacitance	151
3.7	Parallel Resonance	153
3.7.1	Maximum impedance by adjusting frequency	155
3.7.2	Selectivity and bandwidth	157
3.8	Locus Diagrams	159
3.8.1	Impedance locus of series connected elements	160
3.8.2	Admittance locus of series connected elements	160
3.8.3	Admittance locus of parallel connected elements	162
3.8.4	Impedance locii of parallel connected elements	163
3.8.5	Current locus of a parallel circuit with one variable branch .	163
3.8.6	Inversion of circle	165
3.9	Magnetically Coupled Circuits	168
3.9.1	Sinusoidal steady state analysis of magnetically coupled circuits	169
3.9.2	The linear transformer	172
3.9.3	The ideal transformer	176
	<i>Problems</i>	181

CHAPTER 4**Three Phase Circuits**

4.1	Introduction	189
4.2	Advantages of Three Phase Over Single Phase	189
4.3	Generation of Three Phase Voltages	190
4.4	Interconnection of Three Phase Windings	192
4.4.1	The star connection	192
4.4.2	The delta connection	194
4.5	Analysis of 3 Phase Networks	196
4.5.1	Balanced star connected load supplied from balanced 3 phase 4 wire supply	197
4.5.2	Balanced star connected load supplied from a balanced 3 phase 3 wire supply	198
4.5.3	Power in a star connected system	202
4.5.4	Balanced Δ – connected load connected to a 3 – phase balanced supply	203
4.5.5	Power in a Δ – connected balanced system	205
4.6	Unbalanced Three Phase Network	208
4.6.1	Unbalanced star connected load supplied from a 3 – phase balanced 4 – wire supply	208
4.6.2	Unbalanced Δ – connected load	209
4.6.3	Unbalanced star connected load supplied from a 3 phase balanced 3 wire supply	211
4.7	Measurement of Three Phase Power	216
4.7.1	Two wattmeter method	216
4.7.2	Wattmeter readings and power factor in a balanced load	218
	<i>Problems</i>	226

CHAPTER 5**Network Topology**

5.1	Introduction	229
5.2	The Concept of a Network Graph	229

5.3	Chords or Links	235
5.3.1	Incidence matrix (A)	235
5.3.2	Circuit matrix or tie set matrix B	238
5.3.3	Cutset matrix Q	241
5.4	Formulation of Network Equations	243
5.4.1	A typical branch of a network	244
5.4.2	Node voltage equations	245
5.4.3	Loop current equations	249
5.4.4	Cutset equations	255
	<i>Problems</i>	262

CHAPTER 6

Network Theorems

6.1	Introduction	265
6.2	General Network Equations	265
6.3	Superposition Theorem	268
6.4	Thevenin's Theorem	274
6.5	Norton's Theorem	276
6.6	Millman's Theorem	286
6.7	Reciprocity Theorem	289
6.8	Compensation Theorem	291
6.9	Tellegen's Theorem	296
6.10	Maximum Power Transfer Theorem	301
6.10.1	When source has internal resistance and the load is purely resistive	301
6.10.2	When source has an impedance and the load has variable impedance	302
6.10.3	When source has impedance and the load is purely resistive	303
	<i>Problems</i>	309

CHAPTER 7**Differential Equations and Initial Conditions in RLC Networks**

7.1	Introduction	316
7.2	Formulation of Network Equations	316
7.3	Duality	320
7.4	Initial Conditions in Networks	326
	7.4.1 Behaviour of R, L and C at $t = 0$	327
	7.4.2 Behaviour of R, L and C at $t = \infty$	329
	7.4.3 Special cases	339
	<i>Problems</i>	348

CHAPTER 8**Time Response of R L C Networks**

8.0	Response of R L C Networks	356
8.1	Types of Energy Sources	356
8.2	Response of RL Networks	359
	8.2.1 Internal energy excitation	359
	8.2.2 Unit impulse excitation	361
	8.2.3 Unit step excitation	362
	8.2.4 Sinusoidal excitation	366
8.3	Response of RC Networks	368
	8.3.1 Internal energy excitation	369
	8.3.2 Impulse excitation	370
	8.3.3 Unit step excitation	371
	8.3.4 Sinusoidal excitation	373
8.4	Response of RLC Networks	381
	8.4.1 Internal energy excitation	381
	8.4.2 Impulse excitation	390
	8.4.3 Unit step excitation	391
	8.4.4 Sinusoidal excitation	394
	<i>Problems</i>	399

CHAPTER 9

Laplace Transform Method of Analysis of Networks

9.1	Introduction	411
9.2	The Laplace Transformation	412
9.3	Laplace Transform of Some Important Time Functions	413
9.4	Some Theorems of Laplace Transformation	415
9.5	Waveform Synthesis	434
9.6	Gate Function	438
9.7	Periodic Function	441
9.8	Application to Solution of Differential Equations	444
9.9	Heaviside's Partial Fraction Expansion Technique	445
9.10	Application to Networks	449
9.11	Transform Networks	452
	9.11.1 Resistance	452
	9.11.2 Inductance	452
	9.11.3 Capacitance	454
	9.11.4 Solution of transform networks	455
9.12	Transfer Function	461
	9.12.1 Poles and zeroes of transfer function	464
	9.12.2 Significance of poles and zeros	466
9.13	Network Functions	469
	9.13.1 Restrictions on poles and zeros of driving point functions	470
	9.13.2 Restrictions on locations of poles and zeros of transfer functions	473
	<i>Problems</i>	478

CHAPTER 10

Two Port Networks

10.1	Introduction	487
10.2	Two Port Networks	488
10.3	Open Circuit Impedance Parameters	489

10.4	Short Circuit Admittance Parameters	490
10.5	Transmission Parameters	495
10.6	Hybrid Parameters or h – Parameters	496
10.7	Relationships Between Different Sets of Parameters	499
10.7.1	Relation between y and z – parameters	499
10.7.2	Transmission parameters to z – parameters	500
10.7.3	h – parameters to z – parameters	500
10.7.4	Inverse hybrid parameters to z – parameters	501
10.8	Reciprocity and Symmetry	502
10.9	Interconnection of Two Port Networks	510
10.9.1	Cascade connection of networks	510
10.9.2	Series connection networks	514
10.9.3	Parallel connection of networks	516
10.9.4	Series parallel connections	519
10.9.5	Parallel – series connection	521
	<i>Problems</i>	530

CHAPTER 11

Network Filters and Attenuators

11.1	Introduction	538
11.2	Symmetrical Networks	538
11.2.1	Image impedances of networks	539
11.2.2	Characteristic impedance of symmetrical networks	541
11.3	Measure of Attenuation : Neper and Decibel	543
11.4	Propagation Constant	545
11.5	Propagation Constant of Symmetrical Networks	546
11.6	Filter Characteristics	548
11.7	Nature of Characteristic Impedance in Pass and Stop Bands	551
11.8	Constant K – Filters	552
11.8.1	Constant – K low pass filter	552
11.8.2	Phase shift of a constant – K LP filter	554
11.8.3	Attenuation of a constant– K LP filter	554
11.8.4	Characteristic impedance of a constant – K LP filter	555
11.8.5	Constant – K high pass filter	555

11.9	m-Derived Filters	557
11.9.1	m-Derived T-filter	558
11.9.2	m-Derived π -filter	559
11.9.3	m-Derived low pass filter	560
11.9.4	m-Derived high pass filter	564
11.9.5	Terminating half or L – section	567
11.10	Bandpass Filters	571
11.10.1	Bandpass constant K – filter	571
11.10.2	Bandpass m-derived filter	574
11.11	Bandstop or Band Elimination Filter	577
11.11.1	Constant K bandstop filter	577
11.11.2	m-Derived bandstop filter	579
11.12	Attenuators	592
11.12.1	Symmetrical attenuators	592
11.12.2	Symmetrical T – attenuator	592
11.12.3	Symmetrical π – attenuator	593
11.12.4	Symmetrical bridged T – attenuator	594
11.12.5	Symmetrical lattice attenuator	597
	<i>Problems</i>	600

CHAPTER 12

Fourier Series and Fourier Transforms

12.1	Introduction	602
12.2	Fourier Series	602
12.3	Convergence of Fourier Series	607
12.4	Symmetry Conditions in Fourier Series	608
12.4.1	Even function symmetry	609
12.4.2	Odd function symmetry	612
12.4.3	Halfwave or rotation symmetry	613
12.4.4	Quarterwave symmetry	616
12.4.5	Concealed symmetry	618
12.5	Complex Fourier Series	620
12.5.1	Some comments about complex fourier series	623

12.6	Fourier Transforms	629
12.6.1	Existence of the fourier transform	631
12.7	Fourier Transform Properties	639
12.8	Application to Networks	654
12.8.1	Periodic input functions	654
12.8.2	Pulse input functions	655
	<i>Problems</i>	656
	Answers to Problems	663
	Multiple Choice Questions (MCQs) for Competitive Examinations	687
	Answers to MCQs for Competitive Examinations	805
	MCQs from Gate Examination, Yearwise from 2004 to 2014	811