

# Contents

---

<i>Preface to Fourth Edition</i> .....	(vii)
<i>Symbols</i> .....	(xvii)
<i>Brief History of Electronics</i> .....	(xxi)

## Chapter 1

<b>PN Junction Diode and its Applications</b>	<b>1-90</b>
1.1 Review of Semiconductor Physics .....	2
1.1.1 Energy Levels and Energy Bands .....	2
1.1.2 The Bohr Atom .....	4
1.1.3 Effective Mass.....	4
1.1.4 Atomic Energy Levels.....	7
1.1.5 Photon Nature of Light.....	8
1.1.6 Ionization Potential .....	9
1.1.7 Collisions of Electrons with Atoms.....	9
1.1.8 Metastable States.....	12
1.1.9 Wave Properties of Matter .....	12
1.1.10 Schrodinger Equation.....	12
1.1.11 Wave Function .....	14
1.1.12 Electronic Configuration.....	15
1.1.13 Types of Electron Emission .....	16
1.2 n-Type and p-Type Semiconductors.....	23
1.2.1 n-Type or Donor Type Semiconductors.....	23
1.2.2 p-Type or Acceptor Type Semiconductors .....	23
1.3 Mass Action Law.....	24
1.4 Continuity Equation.....	24
1.5 The Hall Effect .....	26
1.6 Fermi Level in Intrinsic and Extrinsic Semiconductors .....	29
1.6.1 Fermi Level .....	29
1.6.2 The Intrinsic Concentration.....	30
1.6.3 Carrier Concentrations in a Semiconductor .....	30
1.6.4 Fermi Level in Intrinsic Semiconductor.....	31
1.7 p-n Diode Equation.....	33
1.8 Volt-Ampere (V-I) Characteristics .....	35

---

1.9	Temperature Dependence of V-I Characteristics.....	36
1.10	Ideal Vs Practical.....	40
1.11	Diode Equivalent Circuits.....	42
1.12	Break Down Mechanisms in Semiconductor Diodes .....	44
1.12.1	Avalanche Breakdown .....	44
1.12.2	Zener Breakdown .....	44
1.12.3	Thermal Breakdown.....	44
1.13	Zener Diode Characteristics .....	45
1.14	p-n Junction Diode as Rectifier .....	46
1.15	Half-Wave Rectifier.....	46
1.15.1	Maximum or Peak Current.....	47
1.15.2	Reading of D.C. Ammeter.....	47
1.15.3	Reading of A.C. Ammeter.....	48
1.15.4	Peak Inverse Voltage.....	48
1.15.5	Regulation .....	50
1.15.6	Ripple Factor.....	52
1.15.7	Ratio of Rectification ( $\eta$ ) .....	54
1.15.8	Transformer Utilization Factor.....	55
1.15.9	Disadvantages of Half Wave Rectifier.....	56
1.15.10	Power Supply Specifications.....	56
1.16	Ripple Factor .....	56
1.17	Full Wave Rectifier (FWR).....	58
1.17.1	Ripple Factor.....	60
1.17.2	Regulation for FWR.....	60
1.17.3	Ratio of Rectification .....	61
1.17.4	Transformer Utilization Factor .....	62
1.17.5	Peak Inverse Voltage for Full Wave Rectifier .....	62
1.17.6	D.C. Saturation.....	62
1.18	Bridge Rectifiers.....	63
1.18.1	Advantages of Bridge Rectifier.....	63
1.18.2	Disadvantages .....	63
1.19	The Harmonic Components in Rectifier Circuit.....	64

1.20 Inductor Filter .....	65
1.20.1 Ripple Factor .....	66
1.20.2 Regulation .....	67
1.21 L-Section Filter .....	69
1.21.1 Ripple Factor in LC Filter .....	70
1.21.2 Bleeder Resistance .....	71
1.21.3 Swinging Choke .....	72
1.22 $\pi$ -Section Filter .....	74
1.22.1 $\pi$ -Section Filter with a Resistor Replacing the Inductor .....	74
1.22.2 Expression for Ripple Factor of $\pi$ -Section Filter .....	75
1.23 Use of Zener Diode as Regulator .....	78
1.23.1 Zener Voltage Regulator Circuit .....	80
1.23.2 Shunt Regulator .....	80
<i>Summary</i> .....	84
<i>Objective Type Questions</i> .....	85
<i>Essay Type Questions</i> .....	86
<i>Multiple Choice Questions</i> .....	87
<i>Conceptual Questions (Interview Questions)</i> .....	89

## Chapter 2

<b>Transistor and FET Characteristics</b>	<b>91-134</b>
2.1 Transistor Construction .....	92
2.1.1 Grown Type .....	92
2.1.2 Alloy Type .....	92
2.1.3 Manufacture of Grown Junction Transistor .....	92
2.1.4 Diffusion Type of Transistor Construction .....	93
2.1.5 Epitaxial Type .....	93
2.2 Bipolar Junction Transistor (BJT) .....	93
2.3 Transistor as an Amplifier .....	94
2.4 Types of Transistor Configurations .....	95
2.4.1 Common Base Configuration (C.B) .....	95
2.4.2 Common Emitter Configuration (C.E) .....	97
2.4.3 Common Collector Configuration (C.C) .....	103
2.5 Limits of Operation .....	105

2.6	BJT Specifications.....	107
2.7	The Junction Field Effect Transistor (FET or JFET).....	108
2.7.1	JFET .....	108
2.7.2	n-Channel JFET .....	109
2.7.3	p-Channel JEET .....	109
2.7.4	FET Structure .....	110
2.7.5	FET Operation.....	110
2.7.6	Pinch off Region.....	114
2.8	JFET Volt-Ampere Characteristics.....	115
2.9	FET as a Voltage Variable Resistor.....	118
2.10	Comparison between BJT and FET .....	118
2.11	MOSFET .....	119
2.11.1	Depletion MOSFET .....	120
2.11.2	Enhancement MOSFET .....	123
2.11.3	MOSFET Operation .....	125
2.11.4	MOSFET Characteristics .....	126
	<i>Summary</i> .....	129
	<i>Objective Type Questions</i> .....	130
	<i>Essay Type Questions</i> .....	131
	<i>Multiple Choice Questions</i> .....	131

**Chapter 3**

<b>Biasing and Stabilization</b>	<b>135-168</b>	
3.1	Operating Point.....	136
3.2	DC and AC Load Lines .....	138
3.3	Need for Biasing/Importance of Biasing .....	138
3.4	Fixed Bias Circuit or (Base Bias Circuit ) .....	139
3.5	Collector to Base Bias circuit .....	140
3.6	Self Bias or Emitter Bias Circuit .....	142
3.7	Bias Stability.....	143
3.8	Stabilization Against Variations in $I_{CO}$ and $V_{BE}$ and $\beta$ .....	144

3.9 Bias Compensation .....	145
3.9.1 Diode Compensation for $V_{BE}$ .....	147
3.10 Thermal Runaway .....	147
3.11 Condition for Thermal Stability in CE Configuration .....	154
3.11.1 Derivation for Condition for Thermal Stability for CE Configuration .....	154
3.12 Biasing of FET .....	156
3.12.1 Fixed Bias Circuit .....	157
3.12.2 Self Bias Circuit .....	158
3.12.3 Self Bias with External Voltage .....	159
3.12.4 Source Self Bias .....	160
3.13 Biasing of Zero Current Drift .....	160
3.14 Biasing Against Device Variation .....	162
<i>Summary</i> .....	164
<i>Objective Type Questions</i> .....	165
<i>Essay Type Questions</i> .....	165
<i>Multiple Choice Questions</i> .....	166
<i>Conceptual Questions (Interview Questions)</i> .....	167

## Chapter 4

<b>Small Signal Analysis of FET and BJT Amplifiers</b>	<b>169-198</b>
4.1 BJT Modeling using h-parameters .....	170
4.2 Determination of h-Parameters from Transistor Characteristics .....	170
4.3 Measurement of h-Parameters .....	171
4.4 Analysis of CE, CB and CC Configurations using h-Parameters .....	173
4.4.1 Input Impedance ( $Z_i$ ) .....	174
4.4.2 Voltage Gain ( $A_V$ ) .....	175
4.4.3 Output Admittance ( $Y_o$ ) .....	175
4.4.4 Voltage Gain ( $A_{V_S}$ ) Considering Source Resistance ( $R_S$ ) .....	176
4.4.5 Current Gain ( $A_{I_S}$ ) Considering Source Resistance .....	176
4.4.6 Power Gain ( $A_p$ ) .....	177
4.5 Comparison of CE, CB, CC Configurations using h-parameters .....	178
4.6 Simplified Transistor Hybrid Model .....	180

4.7	Miller's Theorem.....	182
4.7.1	Dual of Miller's Theorem .....	183
4.8	Small Signal Model of JFET .....	185
4.9	Small Signal Model of MOSFET Amplifiers.....	186
4.10	Small Signal Analysis of Common Source JFET Amplifier .....	188
4.11	Small Signal Analysis of Common Drain FET Amplifier.....	190
	<i>Summary</i> .....	193
	<i>Objective Type Questions</i> .....	193
	<i>Essay Type Questions</i> .....	194
	<i>Multiple Choice Questions</i> .....	195
	<i>Conceptual Questions (Interview Questions)</i> .....	197

**Chapter 5**

	<b>Special Purpose Electronic Devices</b>	<b>199-228</b>
5.1	The Tunnel Diode.....	200
5.1.1	Principle of Operation .....	200
5.1.2	Characteristics of a Tunnel Diode.....	201
5.2	Varactor Diode .....	203
5.3	Schottky Barrier Diode.....	204
5.4	Silicon Controlled Rectifier.....	207
5.4.1	Annular Type of Construction of SCR.....	207
5.4.2	Static Characteristics .....	208
5.4.3	Analysis of the Operation of SCR.....	209
5.4.4	Anode to Cathode Voltage - Current Characteristics.....	212
5.5	DIAC .....	213
5.5.1	Diagram for Basic Construction and Symbol.....	213
5.5.2	Characteristics of DIAC .....	213
5.6	TRIAC .....	214
5.6.1	Construction .....	215
5.6.2	Characteristics .....	215
5.7	Unijunction Transistor (UJT) .....	215
5.7.1	UJT Construction and Operation.....	216
5.7.2	V - I Characteristics of UJT .....	218
5.7.3	Applications of UJT .....	219

5.8	Semiconductor Photo Devices .....	219
5.8.1	Light Dependent Resistors (LDR).....	219
5.8.2	Light Emitting Diode (LED).....	221
5.8.3	Photo Diodes .....	225
5.8.4	Photo Transistors.....	226
	<i>Summary</i> .....	227
	<i>Essay Type Questions</i> .....	227
	<i>Multiple Choice Questions</i> .....	227
	<i>Conceptual Questions (Interview Questions)</i> .....	228

## Chapter 6

### Feedback Amplifiers

6.1	Feedback Amplifiers.....	230
6.2	Classification of Amplifiers .....	230
6.2.1	Voltage Amplifier .....	231
6.2.2	Current Amplifier .....	231
6.2.3	Transconductance Amplifier.....	232
6.2.4	Trans Resistance Amplifier .....	232
6.3	Feedback Concept .....	233
6.4	Types of Feedback.....	235
6.5	Effect of Negative Feedback on Transfer Gain .....	235
6.5.1	Reduction in Gain .....	236
6.5.2	Increase in Bandwidth.....	236
6.5.3	Reduction in Distortion .....	237
6.5.4	Feedback to Improve Sensitivity.....	238
6.5.5	Frequency Distortion .....	238
6.5.6	Band Width .....	239
6.5.7	Sensitivity of Transistor Gain .....	239
6.5.8	Reduction of Nonlinear Distortion .....	240
6.5.9	Reduction of Noise .....	240
6.6	Transfer Gain with feedback .....	240
6.6.1	Loop Gain.....	242
6.7	Classification of Feedback Amplifiers .....	244

6.8	Effect of Feedback on Input Resistance .....	245
6.8.1	Input Resistance with Shunt Feedback.....	245
6.8.2	Input Impedance with Series Feedback.....	247
6.9	Effect of Negative Feedback on $R_o$ .....	248
6.9.1	Voltage Series Feedback .....	248
6.9.2	Current Shunt Feedback.....	249
6.10	Analysis of Feedback Amplifiers .....	254
6.10.1	Voltage Series Feedback .....	254
6.10.2	Current Shunt Feedback.....	259
6.10.3	Current Series Feedback.....	265
6.10.4	Current Series Feedback (Trans Conductance Amplifier) .....	266
6.10.5	Voltage Shunt Feedback (Trans Resistance Amplifier) .....	269
	<i>Summary</i> .....	273
	<i>Objective Type Questions</i> .....	273
	<i>Essay Type Questions</i> .....	274
	<i>Multiple Choice Questions</i> .....	275
	<i>Conceptual Questions (Interview Questions)</i> .....	276

## Chapter 7

### Oscillators

7.1	Oscillators.....	278
7.1.1	Performance Measures of Oscillator Circuits .....	278
7.2	Sinusoidal Oscillators .....	281
7.3	Barkhausen Criterion .....	281
7.4	R – C Phase-shift Oscillator (using JFET).....	282
7.4.1	To find the $\beta$ of the RC Phase-shift Network (JFET) .....	283
7.5	Transistor RC Phase-shift Oscillator .....	285
7.6	A General form of LC Oscillator Circuit .....	288
7.7	Loop Gain .....	288
7.7.1	For Hartley Oscillator .....	290
7.7.2	For Colpitts Oscillator.....	290
7.8	Wien Bridge Oscillator .....	291
7.9	Expression for $f$ .....	292
7.10	Thermistor .....	293

7.11 Sensistor.....	293
7.12 Amplitude Stabilization.....	293
7.13 Applications .....	294
7.14 Resonant Circuit Oscillators.....	294
7.15 Crystal Oscillators .....	295
7.16 Frequency Stability .....	296
7.17 Frequency of Oscillations for Parallel Resonance Circuit .....	297
7.18 1 MHz FET Crystal Oscillator Circuit.....	297
<i>Summary</i> .....	299
<i>Objective Type Questions</i> .....	299
<i>Essay Type Questions</i> .....	300
<i>Multiple Choice Questions</i> .....	301
<i>Conceptual Questions (Interview Questions)</i> .....	302
<i>Additional Objective Type Questions (Chapter 1-7)</i> .....	303
<i>Answers to Additional Objective Type Questions</i> .....	304
<i>Appendices</i> .....	305
<i>Appendix-I Colour Codes for Electronic Components</i> .....	306
<i>Appendix-II Resistor and Capacitor Values</i> .....	309
<i>Appendix-III Capacitors</i> .....	312
<i>Appendix-IV Inductors</i> .....	318
<i>Appendix-V Miscellaneous</i> .....	322
<i>Appendix-VI Circuit Symbols</i> .....	332
<i>Appendix-VII Unit Conversion Factors</i> .....	334
<i>Appendix-VIII American Wire Gauge Sizes and Metric Equivalents</i> .....	337
<i>Answers to Objective Type and Multiple Choice Questions</i> .....	339
<b><i>MCQs from Gate Examination, Yearwise from 1996 to 2012</i></b> .....	<b>347</b>
<b><i>Index</i></b> .....	<b>387</b>