

# 1

## Single Stage Amplifiers

---

*In this Unit,*

- ◆ Single stage amplifiers in the three configurations of C.E, C.B, C.C, with design aspects are given.
- ◆ Using the design formulae for  $A_v$ ,  $A_p$ ,  $R_p$ ,  $R_o$  etc., the design of single stage amplifier circuits is to be studied.
- ◆ Single stage JFET amplifiers in C.D, C.S and C.G configurations are also given.
- ◆ The Hybrid -  $\pi$  equivalent circuit of BJT, expressions for Transistor conductances and capacitances are derived.
- ◆ Miller's theorem, definitions for  $f_\beta$  and  $f_T$  are also given.
- ◆ Numerical examples, with design emphasis are given.

## Introduction

An electronic amplifier circuit is one, which modifies the characteristics of the input signal, when delivered the output side. The modification in the characteristics of the input signal can be with respect to voltage, current, power or phase. Any one or all these characteristics power, or phase may be changed by the amplifier circuit.

### 1.1 CLASSIFICATION OF AMPLIFIERS

Amplifier circuits are classified in different ways as indicated below :

#### Types of Classification is Based on

- (a) Frequency range
- (b) Type of coupling
- (c) Power delivered/conduction angle
- (d) Signal handled.

#### (a) Frequency Range

AF (Audio Freq.)	: 40 Hzs – 15/20 kHz
RF (Radio Freq.)	: > 20 kHz
Video Frequency	: 5 – 8 MHz
VLF (Very Low Freq.)	: 10 – 30 kHz
LF (Low Frequency)	: 30 – 300 kHz
Medium Frequency	: 300 – 3000 kHz
High Frequency	: 3 – 30 MHz
VHF (Very High Freq.)	: 30 – 300 MHz
UHF (Ultra High Freq.)	: 300 – 3000 MHz
SHF (Super High Freq.)	: 3000 – 30,000 MHz

#### (b) Types of Coupling

1. Direct coupled
2. RC coupled
3. Transformer coupled
4. LC Tuned Amplifiers
5. Series fed.

#### (c) Output power delivered/conduction angle

1. Low power (tens of mW or less).
2. Medium power (hundreds of mW).
3. High power (Watts).

Class A	360°
Class B	180°
Class AB	180 – 360°
Class C	< 180°
Class D	Switching type.
Class S	Switching type.

**(d) Type of signal handled**

1. Large signal
2. Small signal

In addition to voltage amplification  $A_V$ , current amplification  $A_I$  or power amplification  $A_P$  is expected from an amplifier circuit. The amplifier circuit must also have other characteristics like High input impedance ( $Z_i$  or  $R_i$ ), Low output impedance ( $Z_o$  or  $R_o$ ), Large Band Width (BW), High signal to Noise Ratio (S/N), and large *Figure of Merit (Gain BW product)*.

In order that the amplified signal is coupled to the load  $R_L$  or  $Z_L$ , for all frequencies of the input signal range, so that maximum power is transferred to the load, (the condition required for maximum power transfer is  $|Z_o| = |Z_L|$  or  $R_o = R_L$ ) coupling the output of amplifier  $V_o$  to load  $R_L$  or  $Z_L$  is important. When reactive elements are used in the amplifier circuit, and due to internal junction capacitances of the active device, the  $Z_i$  and  $Z_o$  of the amplifier circuit change with frequency. As the input signal frequency varies over a wide range, and for all these signals amplification and impedance matching have to be achieved, coupling of the output of the amplifier to the load is important.

Since the gain  $A_V$ ,  $A_I$  or  $A_P$  that can be obtained from a single stage amplifier circuit where only one active device (BJT, JFET or MOSFET) is used, the amplifier circuits are cascaded to get large gain. Multistage amplifier circuits are discussed in the next chapter.

When the frequency of the input signal is high (greater than A.F. range) due to internal junction capacitances of the actual device, the equivalent circuit of the BJT used earlier is not valid. So another model of BJT valid for high frequencies, proposed by Giacoletto is studied in this chapter.

**1.2 DISTORTION IN AMPLIFIERS**

If the input signal is a sine wave the output should also be a true sine wave. But in all the cases it may not be so, which we characterize as distortion. Distortion can be due to the nonlinear characteristic of the device, due to operating point not being chosen properly, due to large signal swing of the input from the operating point or due to the reactive elements L and C in the circuit. Distortion is classified as :

- (a) **Amplitude distortion** : This is also called non linear distortion or harmonic distortion. This type of distortion occurs in large signal amplifiers or power amplifiers. It is due to the nonlinearity of the characteristic of the device. This is due to the presence of new frequency signals which are not present in the input. If the input signal is of 10 KHz the output signal should also be 10 kHz signal. But some harmonic terms will also be present. Hence the amplitude of the signal (rms value) will be different  $V_o = A_V V_i$ . But it will be  $V_o'$ .
- (b) **Frequency distortion** : The amplification will not be the same for all frequencies. This is due to reactive component in the circuit.
- (c) **Phase-shift delay distortion** : There will be phase shift between the input and the output and this phase shift will not be the same for all frequency signals. It also varies with the frequency of the input signal.


In the output signal, all these distortions may be present or any one may be present because of which the amplifier response will not be good.

**Example : 1.1**

The transistor parameters are given as,

$$\begin{array}{llll} h_{ie} = 2 \text{ k} & h_{fe} = 50 & h_{re} = 6 \times 10^{-4} & h_{oe} = 25 \text{ } \mu\text{A/V} \\ h_{ic} = 2 \text{ k} & h_{fc} = -51 & h_{rc} = 1 & h_{oc} = 25 \text{ } \mu\text{A/V} \end{array}$$

Find the individual as well as overall voltage gains and current gains. (Fig. 1.1(a)).

 

**Fig. 1.1 (a) Circuit for Ex : 1.1**

**Solution :**

It is advantageous to start the analysis with the last stage. Compute the current gain first, then the input impedance and voltage gain.

**II stage :** For the second stage  $R_L = R_{e2}$

$$\begin{aligned} A_{I_2} &= \frac{-I_{e2}}{I_{b2}} = \frac{-h_{fc}}{1 + h_{oc}R_{e2}} \\ &= \frac{51}{1 + 25 \times 10^{-6} \times 5 \times 10^3} \\ &= \mathbf{45.3} \end{aligned}$$

$$\begin{aligned} \text{Input impedance } R_{i2} &= h_{ic} + h_{rc} A_{I_2} R_{e2} \\ &= 2 + 45.3 \times 5\text{k} = 228.5 \text{ k.} \end{aligned}$$

$\therefore$  Input Z of the C.C. stage is very high.

Voltage gain of the second stage

$$A_{V_2} = \frac{V_0}{V_2} = A_{I_2} \frac{R_{e2}}{R_{i2}}$$

$$\begin{aligned} \therefore V_0 &= I_{e2} R_{e2}; \\ V_2 &= \text{Input voltage for the second stage} = R_{i2} \cdot I_i \end{aligned}$$

$$\therefore \frac{V_0}{V_2} = \frac{I_0 \cdot R_{e2}}{I_i \cdot R_{i2}}$$

$$\begin{aligned}
 &= A_{I_2} \frac{R_{e_2}}{R_{i_2}} \\
 &= \frac{45.3 \times 5}{228.5} = \mathbf{0.99}
 \end{aligned}$$

**I stage :** For the first stage, the net load resistance in the parallel combination of  $R_{C_1}$  and  $R_{i_2}$  or

$$R_{i_2} = \frac{R_{c_1} \cdot R_{i_2}}{R_{c_1} + R_{i_2}} = \frac{5 \times 228.5}{233.5} = 4.9 \text{ k}\Omega$$

Hence 
$$A_{I_1} = \frac{-I_{C_1}}{I_{b_1}} = \frac{-h_{fe}}{1 + h_{oe}R_{L_1}} = \frac{-50}{1 + 25 \times 10^{-6} \times 4.9 \times 10^3} = -44.5$$

The input impedance of the first stage will also be the input  $Z$  of the two stages since input  $Z$  of the second stage is also considered in determining the value of  $R_{L_1}$ .  $R_{i_1}$  depends on  $R_{L_1}$ .

$$\begin{aligned} \therefore R_{i_1} &= h_{ie} + h_{re} A_{I_1} R_{L_1} \quad (\text{from the standard formula}) \\ &= 2 - 6 \times 10^{-4} \times 44.5 \times 4.9 \end{aligned}$$

$$R_{i_1} = 1.87 \text{ k}\Omega.$$


Voltage gain of the first stage is,

$$\begin{aligned} A_{V_1} &= \frac{V_2}{V_1} = \frac{A_{I_1} \cdot R_{L_1}}{R_{i_1}} \\ &= \frac{-44.5 \times 4.9}{1.87} = -116.6 \end{aligned}$$

$$\begin{aligned} A_I &= \frac{-I_{e_2}}{I_{b_1}} = \frac{-I_{e_2}}{I_{b_2}} \cdot \frac{+I_{b_2}}{I_{c_1}} \cdot \frac{+I_{c_1}}{I_{b_1}} \\ &= -A_{I_2} \cdot \frac{I_{b_2}}{I_{c_1}} \cdot A_{I_1} \end{aligned}$$

In the actual circuit, the current gets branched into  $I_{c_1}$  and  $I_{b_2}$  which depend upon the values of  $R_{C_1}$  and  $R_{i_2}$ . (Fig. 1.1(b)).

$$\begin{aligned} \therefore &(-I_{b_2} + I_{c_1}) R_{c_1} = I_{b_2} \cdot R_{i_2} \\ \therefore &+ I_{b_2} (R_{i_2} + R_{c_1}) = I_{c_1} \cdot R_{c_1} \end{aligned}$$

 

**Fig. 1.1 (b) Current branching**

$$\frac{I_{b2}}{I_{c1}} = \frac{R_{c1}}{R_{c1} + R_{i2}}$$

$$\therefore A_1 = A_{i2} A_{i1} \cdot \frac{R_{c1}}{R_{i2} + R_{c1}}$$

$$= \frac{45.3 \times (-44.5) \times 5}{228.5 + 5}$$

$$A_1 = -43.2$$

$$A_V = \frac{V_0}{V_1} = \frac{V_0}{V_2} \cdot \frac{V_2}{V_1} = A_{V2} \cdot A_{V1}$$

$$A_V = 0.99 \times (-116.6) = -115.$$

$$\frac{I_{b2}}{I_{c1}} = \frac{R_{c1}}{R_{c1} + R_{i2}}$$

### 1.3 ANALYSIS OF CE, CC AND CB AMPLIFIERS

*Small Signal Analysis* means, we assume that the input AC signal peak to peak amplitude is very small around the operating point Q as shown in Fig. 1.2. The swing of the signal always lies in the active region, and so the output is not distorted. In the *Large Signal Analysis*, the swing of the input signal is over a wide range around the operating point. The magnitude of the input signal is very large. Because of this the operating region will extend into the cutoff region and also saturation region.

 


Fig. 1.2 Output characteristics of BJT

1.3.1 COMMON EMITTER AMPLIFIER

Common Emitter Circuit is as shown in the Fig. 1.3. The DC supply, biasing resistors and coupling capacitors are not shown since we are performing an AC analysis.

 


Fig. 1.3 C.E. amplifier

$E_S$  is the input signal source and  $R_S$  is its resistance. The  $h$ -parameter equivalent for the above circuit is as shown in Fig. 1.4.

$$h_{ie} = \left. \frac{V_{be}}{I_b} \right|_{V_{ce}=0} \qquad h_{re} = \left. \frac{V_{be}}{V_{ce}} \right|_{I_b=0}$$

$$h_{oe} = \left. \frac{I_c}{V_{ce}} \right|_{I_b=0} \qquad h_{fe} = \left. \frac{I_c}{I_b} \right|_{V_{ce}=0}$$

The typical values of the  $h$ -parameter for a transistor in Common Emitter Configuration are,  
 $h_{ie} = 4 \text{ k}\Omega$ ,

 


Fig. 1.4  $h$ -parameter equivalent circuit

Since,  $h_{ie} = \frac{V_{be}}{I_b}$   
 $V_{be}$  is a fraction of volt 0.2V,  $I_b$  in  $\mu\text{A}$ , 100  $\mu\text{A}$  and so on.  
 $\therefore h_{ie} = \frac{0.2\text{V}}{50 \times 10^{-6}} = 4 \text{ k}\Omega$

$$h_{fe} = I_c/I_b \simeq 100$$

$I_c$  is in mA and  $I_b$  in  $\mu A$ .

$$\therefore h_{fe} \gg 1 \simeq \beta$$

$h_{re} = 0.2 \times 10^{-3}$ . Because, it is the *Reverse Voltage Gain*.

$$h_{re} = \frac{V_{be}}{V_{ce}}$$

and  $V_{ce} > V_{be}$ ;

$$h_{re} = \frac{\text{Input}}{\text{Output}}$$

Output is  $\gg$  input, because amplification takes place. Therefore  $h_{re} \ll 1$ .

$$h_{oe} = 8 \mu\bar{O} \quad \text{and} \quad h_{oe} = \frac{I_c}{V_{ce}}$$

### 1.3.2 INPUT RESISTANCE OF THE AMPLIFIER CIRCUIT ( $R_i$ )

The general expression for  $R_i$  in the case of Common Emitter Transistor Circuit is

$$R_i = h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + \frac{1}{R_L}} \quad \dots(1.1)$$

For Common Emitter Configuration,

$$R_i = h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + \frac{1}{R_L}} \quad \dots(1.2)$$

$R_i$  depends on  $R_L$ . If  $R_L$  is very small,  $\frac{1}{R_L}$  is large, therefore the denominator in the second term is large or it can be neglected.

$$\therefore R_i \cong h_{ie}$$

If  $R_L$  increases, the second term cannot be neglected.

$$R_i = h_{ie} - (\text{finite value})$$

Therefore,  $R_i$  decreases as  $R_L$  increases. If  $R_L$  is very large,  $\frac{1}{R_L}$  will be negligible compared

to  $h_{oe}$ . Therefore,  $R_i$  remains constant. The graph showing  $R_i$  versus  $R_L$  is indicated in Fig. 1.5.  $R_i$  is not affected by  $R_L$  if  $R_L < 1 \text{ k}\Omega$  and  $R_L > 1 \text{ M}\Omega$  as shown in Fig. 1.5.



 


Fig. 1.5 Variation of  $R_i$  with  $R_L$

$R_i$  varies with frequency  $f$  because h-parameters will vary with frequency.  $h_{fe}$ ,  $h_{re}$  will change with frequency  $f$  of the input signal.

**1.3.3 OUTPUT RESISTANCE OF AN AMPLIFIER CIRCUIT ( $R_o$ )**

For Common Emitter Configuration,

$$R_o = \frac{1}{h_{oe} - \left( \frac{h_{re} h_{fe}}{h_{ie} + R_s} \right)} \quad \dots(1.3)$$

$R_s$  is the resistance of the source. It is of the order of few hundred  $\Omega$ .  $R_o$  depends on  $R_s$ . If  $R_s$  is very small compared to  $h_{ie}$ ,

$$R_o = \frac{1}{h_{oe} - \frac{h_{re} h_{fe}}{h_{ie}}} \quad (\text{independent of } R_s) \quad \dots(1.4)$$

Then,  $R_o$  will be large of the order of few hundred  $k\Omega$ . If  $R_s$  is very large, then

$$R_o \simeq \frac{1}{h_{oe}} \simeq 150 \text{ k}\Omega.$$

The graph is as shown in Fig. 1.6.

 


Fig. 1.6 Variation of  $R_o$  with  $R_s$

### 1.3.4 CURRENT GAIN ( $A_i$ )

$$A_i = \frac{-h_{fe}}{1 + h_{oe}R_L} \quad \dots(1.5)$$

If  $R_L$  is very small,  $A_i \simeq h_{fe} \simeq 100$ . So, Current Gain is large for Common Emitter Configuration. As  $R_L$  increases,  $A_i$  drops and when  $R_L = \infty$ ,  $A_i = 0$ . Because, when  $R_L = \infty$ , output current  $I_o$  or load current  $I_L = 0$ . Therefore,  $A_i = 0$ . Variation of  $A_i$  with  $R_L$  is shown in Fig. 1.7.

 


Fig 1.7 Variation of  $A_i$  with  $R_L$

### 1.3.5 VOLTAGE GAIN ( $A_v$ )

$$A_v = \frac{-h_{fe}R_L}{h_{ie} + R_L(h_{ie}h_{oe} - h_{fe}h_{re})} \quad \dots(1.6)$$

If  $R_L$  is low, most of the output current flows through  $R_L$ . As  $R_L$  increases, output voltage increases and hence  $A_v$  increases. But if  $R_L \gg \frac{1}{h_{oe}}$ , then the current from the current generator in the *h-parameters* equivalent circuit flows through  $h_{oe}$  and not  $R_L$ .

Then the, Output Voltage =  $h_{fe} \cdot I_b \cdot \frac{1}{h_{oe}}$

( $R_L$  is in parallel with  $h_{oe}$ . So voltage across  $h_{oe} =$  voltage across  $R_L$ ). Therefore,  $V_o$  remains constant as output voltage remains constant (Fig.1.8).

 


Fig. 1.8 Variation of  $A_v$  with  $R_L$

### 1.3.6 POWER GAIN ( $A_P$ )

As  $R_L$  increases,  $A_I$  decreases. As  $R_L$  increases,  $A_V$  also increases.

Therefore, Power Gain which is the product of the two,  $A_V$  and  $A_I$  varies as shown in Fig. 1.9.

$$A_P = A_V A_I$$

 


Fig. 1.9 Variation of  $A_P$  with  $R_L$

Power Gain is maximum when  $R_L$  is in the range  $100 \text{ k}\Omega - 1 \text{ M}\Omega$  i.e., when  $R_L$  is equal to the output resistance of the transistor. Maximum power will be delivered, under such conditions.

Therefore, it can be summarised as, Common Emitter Transistor Amplifier Circuit will have,

1. Low to Moderate Input Resistance ( $300 \Omega - 5 \text{ k}\Omega$ ).
2. Moderately High Output Resistance ( $10 \text{ k}\Omega - 100 \text{ k}\Omega$ ).
3. Large Current Amplification.
4. Large Voltage Amplification.
5. Large Power Gain.
6.  $180^\circ$  phase-shift between input and output voltages.

As the input current  $I_B$ , increases,  $I_C$  increases therefore drop across  $R_C$  increases and  $V_0 = V_{CC} - V_{I_C}$  drop across  $R_C$ . Therefore, there is a phase shift of  $180^\circ$ .

The amplifier circuit is shown in Fig. 1.10.

 


Fig. 1.10 CE amplifier circuit

### 1.3.7 COMMON BASE AMPLIFIER

The circuit diagram considering *only AC* is shown in Fig. 1.11.

 


Fig. 1.11 CB amplifier

$$h_{ib} = \left. \frac{V_{eb}}{I_e} \right|_{V_{cb}=0}$$

$V_{eb}$  is small fraction of a volt.  $I_e$  is in mA. So,  $h_{ib}$  is small.

$$h_{fb} = \left. \frac{I_c}{I_e} \right|_{V_{cb}=0} = -0.99 \text{ (Typical Value)}$$

$$I_c < I_e \quad \therefore \quad h_{fb} < 1$$

$$h_{ob} = \left. \frac{I_c}{V_{cb}} \right|_{I_e=0} = 7.7 \times 10^{-8} \text{ mhos (Typical Value)}$$

$I_c$  will be very small because  $I_e = 0$ . This current flows in between base and collector loop.

$$h_{rb} = \left. \frac{V_{eb}}{V_{cb}} \right|_{I_e=0} = 37 \times 10^{-6} \text{ (Typical Value)}$$

$h_{rb}$  is small, because  $V_{eb}$  will be very small and  $V_{cb}$  is large.

### 1.3.8 INPUT RESISTANCE ( $R_i$ )

$$R_i = h_{ib} - \frac{h_{fb} \cdot h_{rb}}{h_{ob} + \frac{1}{R_L}}; \quad h_{fb} \text{ is -ve} \quad \dots(1.7)$$

when  $R_L$  is small  $< 100 \text{ k}\Omega$ , the second term can be neglected.

$$\therefore \quad R_i = h_{ib} \simeq 30 \text{ }\Omega.$$

when  $R_L$  is very large,  $\frac{1}{R_L}$  can be neglected.

$$R_i = h_{ib} - \frac{h_{fb} \cdot h_{rb}}{h_{ob}}$$

So  $R_i \simeq 500 \Omega$  (Typical value) [ $\because h_{fb}$  is negative]

$$\therefore R_i = h_{ib} + \frac{h_{fb} h_{rb}}{h_{ob}}$$

The variation of  $R_i$  with  $R_L$  is shown in Fig. 1.12.  $R_i$  varies from  $20 \Omega$  to  $500 \Omega$ .

 


Fig. 1.12 Variation of  $R_i$  with  $R_L$

### 1.3.9 OUTPUT RESISTANCE ( $R_o$ )

$$R_o = \frac{1}{h_{ob} - \frac{h_{rb} h_{fb}}{h_{ib} + R_s}} \quad \dots(1.8)$$

If  $R_s$  is small, 
$$R_o = 1 / \left( h_{ob} - \frac{h_{rb} h_{fb}}{h_{ib}} \right)$$

But  $h_{fb}$  is negative.

$$\therefore R_o = \frac{1}{h_{ob} + \frac{h_{rb} h_{fb}}{h_{ib}}}$$

This will be sufficiently large, of the order of  $300 \text{ k}\Omega$ . Therefore, value of  $h_{ob}$  is small. As  $R_s$  increases,  $R_o = \frac{1}{h_{ob}}$  also increases. [This will be much larger because, in the previous case, in the denominator, some quantity is subtracted from  $h_{ob}$ .]

$$\therefore R_o = 12 \text{ M}\Omega$$

The variation of  $R_0$  with  $R_s$  is shown in Fig. 1.13.

 


Fig. 1.13 Variation of  $R_0$  with  $R_s$

1.3.10 CURRENT GAIN ( $A_i$ )

$$A_i = \frac{-h_{fb}}{1 + h_{ob}R_L} \quad \dots( 1.9 )$$

$A_i$  is  $< 1$ . Because  $h_{fe} < 1$ . As  $R_L$  increases,  $A_i$  decreases.  $A_i$  is negative due to  $h_{fb}$ . The variation of  $A_i$  with  $R_L$  is shown in Fig. 1.14.

 


Fig. 1.14 Variation of  $A_i$  with  $R_L$

1.3.11 VOLTAGE GAIN ( $A_v$ )

$$A_v = \frac{-h_{fb}R_L}{h_{ib} + R_L(h_{ib}h_{ob} - h_{fb}h_{rb})} \quad \dots\dots\dots ( 1.10 )$$

As  $R_L$  increases,  $A_v$  also increases. If  $R_L$  tends to zero,  $A_v$  also tends to zero. ( $A_v \rightarrow 0$ , as  $R_L \rightarrow 0$ ). The variation of Voltage Gain  $A_v$  with  $R_L$  is shown in Fig. 1.15.

 


Fig. 1.15 Variation of  $A_v$  with  $R_L$

### 1.3.12 POWER GAIN ( $A_p$ )

$$\text{Power Gain } A_p = A_v \cdot A_i$$

$A_v$  increases as  $R_L$  increases. But  $A_i$  decreases as  $R_L$  increases. Therefore, Power Gain, which is product of both, varies with  $R_L$  as shown in Fig. 1.16.

 


Fig 1.16 Variation of  $A_p$  with  $R_L$

The characteristics of Common Base Amplifier with typical values are as given below.

1. Low Input Resistance (few  $100 \Omega$ ).
2. High Output Resistance ( $M\Omega$ ).
3. Current Amplification  $A_i < 1$ .
4. High Voltage Amplification and No Phase Inversion
5. Moderate Power Gain (30).  $\therefore A_i < 1$ .

### 1.3.13 COMMON COLLECTOR AMPLIFIER

The simplified circuit diagram for AC of a transistor (BJT) in Common Collector Configuration is as shown in Fig. 1.17 (without biasing resistors).

 


Fig. 1.17 CC Amplifier

The *h-parameter* equivalent circuit of transistor in Common Collector Configuration is shown in Fig. 1.18.

 


Fig. 1.18 *h-parameter* equivalent circuit

$$h_{ic} = \left. \frac{V_{bc}}{I_b} \right|_{V_{ec}=0} = 2,780 \, \Omega \text{ (Typical Value)}$$

$$h_{oc} = \left. \frac{I_e}{V_{ec}} \right|_{I_b=0} = 7.7 \times 10^{-6} \text{ mhos (Typical Value)}$$

$$h_{fc} = - \left. \frac{I_e}{I_b} \right|_{V_{ce}=0} = 100 \text{ (Typical value)}$$

$$\therefore I_e \gg I_b.$$

$h_{fc}$  is negative because,  $I_E$  and  $I_B$  are in opposite direction.

$$h_{rc} = \left. \frac{V_{bc}}{V_{ec}} \right|_{I_b=0}; \quad V_{bc} = V_{ec} \text{ (Typical Value)}$$

Because,  $I_B = 0$ , E - B junction is not forward biased.

$$\therefore V_{EB} = 0.$$

For other circuit viz., Common Base and Common Emitter,  $h_r$  is much less than 1.

For Common Collector Configuration,  $h_{rc} \simeq 1$ .

The graphs (variation with  $R_C$ ) are similar to Common Base Configuration.

### Characteristics

1. High Input Resistance  $\simeq 3 \text{ k}\Omega$  ( $R_i$ )
2. Low Output Resistance  $30 \, \Omega$  ( $R_o$ )
3. Good Current Amplification  $A_i \gg 1$
4.  $A_v \leq 1$
5. Lowest Power Gain of all the configurations.

Since,  $A_v < 1$ , the output voltage (Emitter Voltage) follows the input signal variation. Hence it is also known as *Emitter Follower*. The graphs of variation with  $R_L$  and  $R_S$  are similar to Common Base amplifier.




**Example : 1.2**

For the circuit shown in Fig.1.19 estimate  $A_v$ ,  $A_i$ ,  $R_i$  and  $R_o$  using reasonable approximations. The *h-parameters* for the transistor are given as

$$h_{fe} = 100 \quad h_{ie} = 2000 \Omega \quad h_{re} \text{ is negligible} \quad \text{and} \quad h_{oe} = 10^{-5} \text{ mhos}(\Omega^{-1}).$$


$$I_b = 100 \mu\text{A}.$$

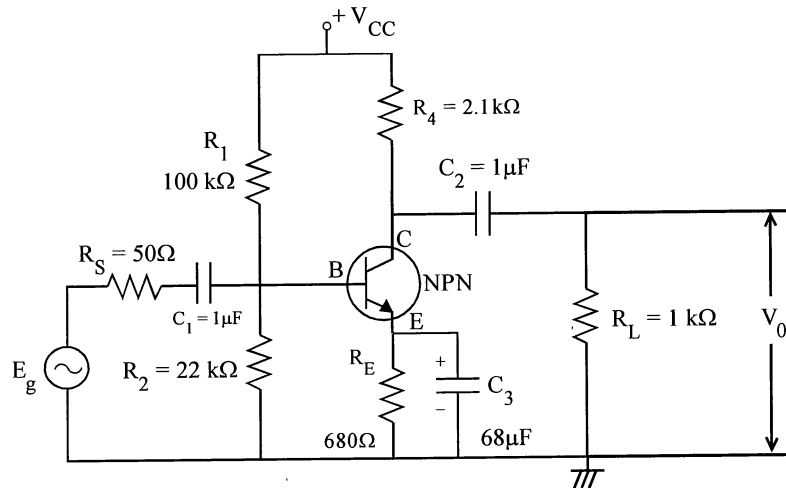

**Fig. 1.19 CE amplifier circuit**

**Solution :**

At the test frequency capacitive reactances can be neglected.  $V_{CC}$  point is at ground because the AC potential at  $V_{CC} = 0$ . So it is at ground.  $R_1$  is connected between base and ground for AC. Therefore,  $R_1 \parallel R_2$ .  $R_4$  is connected between collector and ground. So  $R_4$  is in parallel with  $1/h_{oe}$  in the output. The A.C. equivalent circuit in terms of *h-parameters* of the transistor is shown in Fig. 1.20.

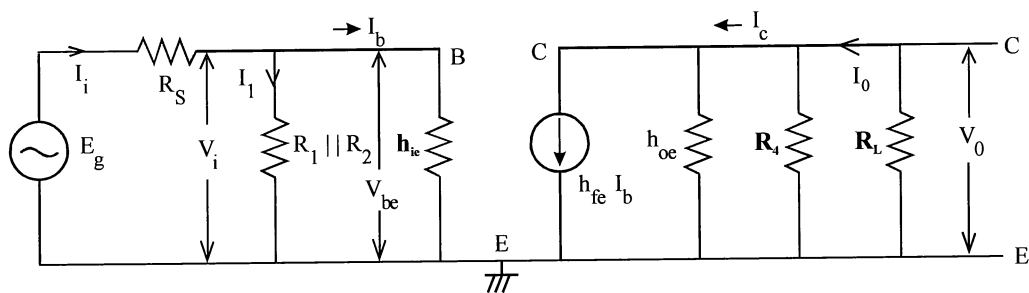

**Fig. 1.20 Equivalent circuit**

The voltage source  $h_{re} V_{ce}$  is not shown since,  $h_{re}$  is negligible. At the test frequency of the input signal, the capacitors  $C_1$  and  $C_2$  can be regarded as short circuits. So they are not shown in the AC equivalent circuit. The emitter is at ground potential. Because  $X_{C_3}$  is also negligible, all the AC passes through  $C_3$ . Therefore, emitter is at ground potential and this circuit is in Common Emitter Configuration.

**Input Resistance ( $R_i$ )**

$R_i$  input resistance looking into the base is  $h_{ie}$  only

$$\text{The expression for } R_i \text{ of the transistor alone} = h_{ie} - \left( \frac{h_{fe} h_{re}}{h_{oe} + \frac{1}{R_L}} \right).$$

$R_L$  is very small and  $h_{re}$  is negligible. Therefore, the second term can be neglected. So  $R_i$  of the transistor alone is  $h_{ie}$ . Now  $R_i$  of the entire amplifier circuit, considering the bias resistors is,

$$\begin{aligned} R_i &= h_{ie} \parallel R_1 \parallel R_2 \\ \therefore \frac{R_1 R_2}{R_1 + R_2} &= \frac{100 \times 22}{100 + 22} = 18 \text{ k}\Omega \\ \therefore R_i &= \frac{18 \times 2}{18 + 2} = 1.8 \text{ k}\Omega \end{aligned}$$

**Output Resistance ( $R_o$ )**

$$R_o = \frac{1}{h_{oe} - \left[ \frac{h_{re} h_{fe}}{h_{ie} + R_s} \right]} \quad \dots(1.11)$$

Because,  $h_{re}$  is negligible,  $R_o$  of the transistor alone in terms of *h-parameters* of the transistor =  $\frac{1}{h_{oe}}$ . Now  $R_o$  of the entire amplifier circuit is,

$$\begin{aligned} \left( \frac{1}{h_{oe}} \parallel R_4 \parallel R_L \right) &= (2.1 \times 10^3) \parallel (100 \text{ k}\Omega) \parallel (1 \text{ k}\Omega) \\ &= 2 \text{ k}\Omega \parallel (1 \text{ k}\Omega) = 0.67 \text{ k}\Omega \end{aligned}$$

**Current Gain ( $A_i$ )**

To determine  $A_i$  the direct formula for  $A_i$  in transistor in Common Emitter Configuration is,  $\frac{-h_{fe}}{1 + h_{oe} R_L}$ .

But this cannot be used because the input current  $I_i$  gets divided into  $I_1$  and  $I_b$ . There is some current flowing through the parallel configuration of  $R_1$  and  $R_2$ . So the above formula cannot be used.

$$\begin{aligned} V_{be} &= I_b \cdot h_{ie} \\ V_{be} &= 10^{-4} \times (2000) = 0.2\text{V. (This is AC Voltage not DC)} \end{aligned}$$

Voltage across  $R_1$   $R_2$  parallel configuration is also  $V_{be}$ .

$$\therefore \text{Current } I_1 = \frac{V_{be}}{50 \times 10^3} = \frac{0.2}{50 \text{ k}\Omega} = 4 \text{ }\mu\text{A.}$$

Therefore total input current,

$$I_i = I_1 + I_b = 4 + 100 = 104 \mu\text{A}.$$

$I_0$  is the current through the  $1 \text{ k}\Omega$  load.

$\frac{1}{h_{oe}} = 100 \text{ k}\Omega$  is very large compared with  $R_4$  and  $R_L$ . Therefore, all the current on the

output side,  $h_{fe} I_b$  gets divided between  $R_4$  and  $R_L$  only.

Therefore current through  $R_L$  is  $I_0$ ,

$$I_0 = h_{fe} I_b \cdot \left[ \frac{R_4}{R_4 + R_L} \right]$$

$$I_0 = 100 \times 10^{-4} \frac{2.1 \times 10^3}{(2.1 \times 10^3 + 10^3)}$$

$$= 6.78 \text{ mA}.$$

Therefore current amplification,

$$A_i = \frac{I_0}{I_i}$$

$$= \frac{6.78 \times 10^{-3}}{104 \times 10^{-6}} = 65.$$

$$A_v = \frac{V_o}{V_i}; \quad V_i = V_{be}$$

$$V_o = -I_0 \cdot R_L$$

$$= (-6.78 \times 10^3) \times (10^3)$$

$$= -6.78 \text{ V}$$

Because, the direction of  $I_0$  is taken as entering into the circuit. But actually  $I_0$  flows down, because  $V_o$  is measured with respect to ground.

$$\therefore A_v = \frac{-6.78}{0.2}$$


$$= -33.9$$

Negative sign indicates that there is phase shift of  $180^\circ$  between input and output voltages, i.e. as base voltage goes more positive, (it is NPN transistor), the collector voltage goes more negative.

**Example : 1.3**

For the circuit shown, in Fig. (1.21), estimate  $A_v$  and  $R_i$ .  $\frac{1}{h_{oe}}$  is large compared with the load seen by the transistor. All capacitors have negligible reactance at the test frequency.


$$h_{ie} = 1 \text{ k}\Omega, h_{fe} = 99 \quad h_{re} \text{ is negligible.}$$

 

**Fig. 1.21 AC amplifier circuit (Ex : 1.2)**

**Solution :**

The same circuit can be redrawn as,

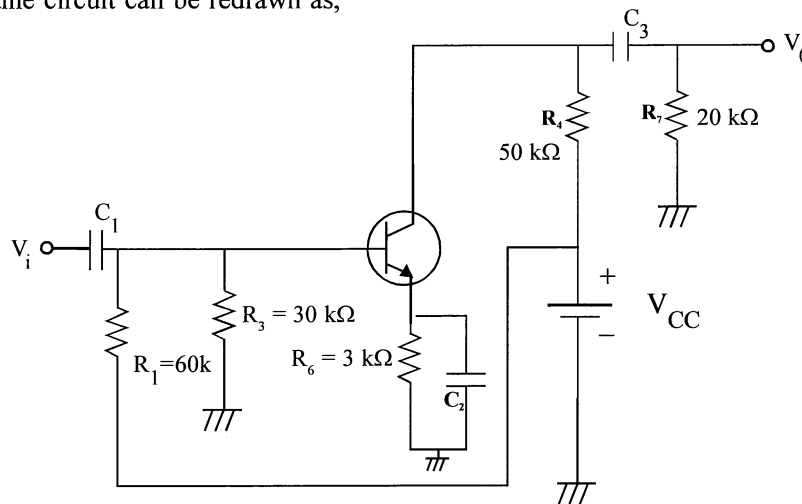

**Fig. 1.22 Redrawn circuit of AC amplifier**

In the second circuit also,  $R_4$  is between collector and positive of  $V_{CC}$ .  $R_1$  is between  $+V_{CC}$  and base. Hence both the circuits are identical. Circuit in Fig. 1.21 is same as circuit in Fig. 1.22. In the AC equivalent circuit, the direct current source should be shorted to ground. Therefore,  $R_4$  is between collector and ground and  $R_1$  is between base and ground. Therefore,  $R_4$  is in parallel with  $R_7$  and  $R_1$  is in parallel with  $R_3$  (Fig. 1.23).

 


Fig. 1.23 *h* - Parameter equivalent circuit

$$R_2 \parallel R_3 = \frac{60 \times 30}{60 + 30} = \frac{1800}{90} = 20 \text{ k}\Omega.$$

$$R_4 \parallel R_7 = R_L = \frac{5 \times 20}{5 + 20} = 4 \text{ k}\Omega.$$

Therefore, the circuit reduces to, (as shown in Fig. 1.24).

 


Fig. 1.24 *Simplified circuit of Fig. 1.23*

$$I_b = \frac{V_i}{h_{ie}} \quad (\because h_{re} \text{ is negligible})$$

$$I_c = h_{fe} I_b = \frac{h_{fe} \cdot V_i}{h_{ie}}$$

$$\therefore V_0 = -I_c \cdot R_L = -\frac{h_{fe} V_i \cdot R_L}{h_{ie}}$$

$$A_v = \frac{V_0}{V_i} = -\frac{h_{fe} R_L}{h_{ie}} = \frac{-99 (14.28 \times 10^3)}{10^3}$$

$$A_v = -400$$

$R_i$  is the parallel combination of  $20 \text{ k}\Omega$  and  $h_{ie}$ .

$$\frac{20 \times 1 \text{ k}\Omega}{20+1} = 950 \Omega$$

**Example : 1.4**

Given a single stage transistor amplifier with  $h$  - parameter as  $h_{ic} = 1.1 \text{ k}\Omega$ ,  $h_{rc} = 1$ ,  $h_{fc} = -51$ ,  $h_{oc} = 25 \mu\text{A/v}$ . Calculate  $A_I$ ,  $A_V$ ,  $A_{V_S}$ ,  $R_i$ , and  $R_o$  for the Common Collector Configuration, with  $R_S = R_L = 10 \text{ k}$ .

**Solution :**

$$A_I = \frac{-h_{fc}}{(1+h_{oc} R_L)} = \frac{51}{1+25 \times 10^{-6} \times 10^4} = 40.8$$

$$R_i = h_{ic} + h_{rc} A_I R_L = 1.1 \times 10^3 + 1 \times 40.8 \times 10^4 = 409.1 \text{ k}\Omega$$

$$A_V = \frac{A_I \cdot R_L}{R_i} = \frac{40.8 \times 10^4}{409.1 \times 10^3} = 0.998$$

$$A_{V_S} = \frac{A_V \cdot R_i}{R_i + R_S} = \frac{0.998 \times 409.1}{419.1} = 0.974$$

$$R_o = \frac{1}{h_{oc} - \frac{h_{fc} \cdot h_{rc}}{h_{ic} + R_S}} = \frac{1}{25 \times 10^{-6} + \frac{51 \times 1}{(1.1+10)10^3}} = \frac{1}{4.625 \times 10^{-3}}$$

$$R_o = 217 \Omega$$

**Example : 1.5**

For any transistor amplifier prove that

$$R_i = \frac{h_i}{1 - h_r A_V}$$

**Solution :**

$$R_i = h_i - \frac{h_f \cdot h_r}{h_o + \frac{1}{R_L}}$$

But  $A_I = \frac{-h_f}{1+h_o \cdot R_L}$

$\therefore R_i = h_i + h_r A_I R_L$  .....(1.12)

$$\therefore A_v = \frac{A_I \cdot R_L}{R_i}$$

$$R_L = \frac{A_v \cdot R_i}{A_I}$$

Substituting this value of  $R_L$  in equation (1.12)

$$R_i = h_i + \frac{h_r \cdot A_I \cdot A_v \cdot R_i}{A_I} = h_i + h_r \cdot A_v \cdot R_i$$

$$R_i [1 - h_r A_v] = h_i \quad \therefore R_i = \frac{h_i}{1 - h_r A_v}$$

### Example : 1.6

For a Common Emitter Configuration, what is the maximum value of  $R_L$  for which  $R_i$  differs by not more than 10% of its value at  $R_L = 0$  ?

$$\begin{aligned} h_{ie} &= 1100 \, \Omega ; & h_{fe} &= 50 \\ h_{re} &= 2.50 \times 10^{-4} ; & h_{oe} &= 25 \, \mu \text{ A/v} \end{aligned}$$

### Solution :

Expression for  $R_i$  is,

$$R_i = h_{ie} - \frac{h_{fe} \cdot h_{re}}{h_{oe} + \frac{1}{R_L}}$$

If  $R_L = 0$ ,  $R_i = h_{ie}$ . The value of  $R_L$  for which  $R_i = 0.9 h_{ie}$  is found from the expression,

$$0.9 h_{ie} = h_{ie} - \frac{h_{fe} \cdot h_{re}}{h_{oe} + \frac{1}{R_L}}$$

$$\text{or} \quad \frac{h_{fe} \cdot h_{re}}{h_{oe} + \frac{1}{R_L}} = h_{ie} - 0.9 h_{ie} = 0.1 h_{ie}$$

$$\frac{h_{fe} \cdot h_{re}}{0.1 h_{ie}} = h_{oe} + \frac{1}{R_L}$$


$$\frac{1}{R_L} = \frac{h_{fe} \cdot h_{re}}{0.1 h_{ie}} - h_{oe} = \frac{h_{fe} h_{re} - 0.1 h_{oe} h_{ie}}{0.1 h_{ie}}$$

$$\text{or} \quad R_L = \frac{0.1 h_{ie}}{h_{fe} h_{re} - 0.1 h_{oe} h_{ie}} = \frac{0.1 \times 1100}{50 \times 2.5 \times 10^{-4} - 0.1 \times 1100 \times 25 \times 10^{-6}}$$

$$R_L = 11.3 \, \text{k}\Omega$$


### 1.4 MILLER'S THEOREM

Fig. 1.25(a) shows an amplifier with a capacitor between input and output terminals. It is called as feedback capacitor. When the gain  $K$  is large, the feedback will change the input  $Z$  and output  $Z$  of the circuit.

 

**Fig. 1.25 (a) Feedback capacitor**

A circuit as shown above is difficult to analyze, because of capacitor. So according to the Miller's theorem, the feedback capacitor can be split into two values, one as connected in the input side and the other on the output side, as shown in Fig. 1.25 (b).

 

**Fig. 1.25 (b) Splitting of feedback capacitor using Miller's theorem.**

#### 1.4.1 MATHEMATICAL PROOF OF MILLER'S THEOREM

The AC current passing through capacitor ( $C$ ) in Fig. 1.25 (a) is

$$I_C = \frac{V_{in} - V_{out}}{\left(\frac{1}{j\omega C}\right)} = \frac{(V_{in} - V_{out})}{-jX_C}$$

$$V_{out} = K V_{in}$$

$$\therefore I_C = \frac{(V_{in} - KV_{in})}{-jX_C} = \frac{V_{in}(1-K)}{-jX_C}$$

$$\begin{aligned} \frac{V_{in}}{I_C} = Z_{in} &= \frac{V_{in}}{\frac{V_{in}(1-K)}{-jX_C}} = \frac{-jX_C}{(1-K)} \\ &= \frac{-j}{2\pi f C(1-K)} \end{aligned}$$

Since  $X_C = \frac{1}{2\pi f C}$



$\frac{V_{in}}{I_C}$  is the input Z as seen from the input terminals.

$$\therefore Z_{in} = \frac{-j}{2\pi f [C(1-K)]}$$

$$\therefore C_{in} = C(1-K)$$

Similarly output capacitance can be derived as follows :

Current in the capacitor,

$$I_C = \frac{V_{out} - V_{in}}{-jX_C} = \frac{V_{out} \left(1 - \frac{V_{in}}{V_{out}}\right)}{-jX_C}$$

$$I_C = \frac{V_{out} \left(1 - \frac{1}{K}\right)}{-jX_C}$$

$$= \frac{V_{out}}{I_C} = Z_{out}$$


$$= \frac{V_{out}}{\frac{V_{out} \left(1 - \frac{1}{K}\right)}{-jX_C}}$$

$$Z_{out} = \frac{-jX_C}{\left(\frac{A-1}{A}\right)} = \frac{-j}{2\pi f C \left(\frac{K-1}{K}\right)}$$

$$\therefore C_{out} \text{ (Miller)} = C \left(\frac{K-1}{K}\right)$$

## FREQUENCY EFFECTS

### LEAD NETWORK (FIG. 1.26)

 

**Fig. 1.26** Lead network

$$I = \frac{V_{in}}{R + \frac{1}{j\omega C}}$$

$$V_0 = I \cdot R = \frac{V_{in} \cdot R}{\left(R + \frac{1}{j\omega C}\right)}$$

$V_0$  leads with respect to  $V_{in}$ . So it is called as *lead network* for the above circuit (Fig. 1.25), at low frequencies,  $X_C = \infty$ .

$\therefore V_0$  is low since (I is low). As  $f$  increases  $X_C$  decreases. Hence I flows, and  $V_0$  increases.

$\therefore$  Gain increases. Hence the frequency response is as shown.

### Cut-off Frequency

 


Fig. 1.27 Frequency response

$$V_{out} = \frac{R}{\sqrt{R^2 + X_C^2}} \cdot V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{R}{\sqrt{R^2 + X_C^2}}$$

Cut-off frequency is the frequency at which  $\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{2}}$ .

This happens when,  $X_C = R$

$$\frac{1}{2\pi f_c C} = R \quad \text{or} \quad \boxed{f_c = \frac{1}{2\pi RC}}$$

Lower cut-off frequency.

### Half Power Point

At  $f = f_c$ ,  $P = \frac{V_{out}^2}{2R}$

Power is half of maximum power when  $V_{out}$  is maximum. Therefore it is also called as half power point.

 


Fig. 1.28 Equivalent circuit

Considering Source Resistance :

$$\frac{V_{out}}{V_{in}} = \frac{R}{\sqrt{(R_S + R_L) + X_c^2}}$$

At  $f_c$ ,  $R_S + R_L = X_c$

$$\therefore f_c = \frac{1}{2\pi(R_S + R_L).C}$$

In the midband frequency region  $X_c \cong 0$ .

$$\therefore \frac{V_{out}}{V_{in}} = \frac{R_L}{R_S + R_L}$$

$$A_{mid} \text{ (midband voltage gain)} = \frac{R_L}{R_S + R_L}$$

**Stiff Coupling**

If  $X_c = 0.1 (R_S + R_L)$  it is called *Stiff Coupling*.

The coupling capacitor must have (or bypass capacitor).

$$X_c = \frac{1}{10} R_E$$

This is known as *Stiff Coupling*.

**Amplifier Analysis**

 


Fig. 1.29 Amplifier circuit

The equivalent circuit from input side, not considering  $R_S$ . (Fig. 1.30).

The equivalent circuit from output side, not considering  $R_L$ .

$$R_{in} = R_1 \parallel R_2 \parallel \beta r_e' \text{ (Not considering } R_S)$$

$$R_{out} \cong R_C \text{ (Not considering } R_L)$$

 


Fig. 1.30 Equivalent circuit

Considering the input side as a load network,

$$f_{in} = \frac{1}{2\pi(R_S + R_{in})C_{in}}$$

Similarly output lead network has cut-off frequency

$$f_{out} = \frac{1}{2\pi(R_{out} + R_L)C_{out}}$$

**Lag Networks**

$$V_0 = I \cdot X_c = \frac{V_i \cdot X_c}{\left(R + \frac{1}{j\omega C}\right)}$$

$$V_0 = \frac{\frac{1}{j\omega C} \cdot V_{in}}{\sqrt{R^2 + X_c^2}}$$

$$V_0 = \frac{-j(V_i / \omega C)}{\sqrt{R^2 + X_c^2}} \text{ therefore it is lag network}$$

$V_0$  lags with respect to  $V_i$ .

$$\frac{V_{out}}{V_{in}} = \frac{X_c}{\sqrt{R^2 + X_c^2}}$$

 


Fig. 1.31 Lag network

 


Fig. 1.32

at  $f_C$ ,  $R = X_C$

$$\therefore f_C = \frac{1}{2\pi RC}$$

Midband gain  $A_{mid} = \frac{R_L}{R_S + R_L}$

**Decibel**

Power gain =  $G = \frac{P_2}{P_1}$

$P_2$  = Output power.

$P_1$  = Input power.

Decibel power gain =  $G' = 10 \log_{10} G$ .

If  $G = 100$ ,  $G' = 10 \log 100 = 20 \text{ db}$ .

If  $G = 2$ ,  $G' = 10 \log 2 = 3.01 \text{ db}$ .

Usually, it is rounded off to 3.

**Negative Decibel**

If  $a < 1$ ,  $a'$  will be negative.

If  $G = \frac{1}{2}$ ,

$$G' = 10 \log \frac{1}{2} = -3.01 \text{ db}$$

	<b>G</b>	<b>G'</b>
If	1	0 db
	10	10 db
	100	20 db
	1000	30 db
	10,000	40 db

**Ordinary Gains Multiply :**

If two stages are there,

 


Fig. 1.33 Cascaded amplifier stages

$$G_1 = \frac{P_2}{P_1}; \quad G_2 = \frac{P_3}{P_2}$$

$$\begin{aligned} \text{Overall gain} \quad G &= \frac{P_3}{P_1} \\ &= \frac{P_2}{P_1} \cdot \frac{P_3}{P_2} \end{aligned}$$

$$G = G_1 G_2$$

*Decibel gains add up.*

### Decibel Voltage Gain

If  $A =$  Normal Voltage Gain  $\frac{V_2}{V_1}$ , decibel voltage gain  $A' = 20 \log A$ .  $A = \frac{V_2}{V_1}$

If  $R_1$  is output resistance,

$$\text{Input power} \quad P_1 = \frac{V_1^2}{R_1}$$

If  $R_2$  is output resistance,  $P_2 = \frac{V_2^2}{R_2}$

$$\therefore \text{Power gain} \quad G = \frac{P_2}{P_1} = \frac{V_2^2}{V_1^2} \cdot \frac{R_1}{R_2}$$

If the impedances are matched, i.e. input resistance


$$R_1 = \text{output resistance } R_2,$$

$$\text{Power gain} \quad G = \frac{V_2^2}{V_1^2} = A^2$$

In decibels,  $10 \log G = G' = 10 \log A^2$ .

In decibels,  $10 \log G = G' = 20 \log A$ .

### Cascaded Stages (Fig. 1.34)

 

*Fig. 1.34 Cascaded stages*

$$A = A_1 \times A_2$$

$$A_1 = A_1' + A_2' \text{ (in decibels)}$$

### Stiff Coupling

When the capacitor is chosen such that,  $X_c = \frac{-R_E}{10}$ , it is called as stiff coupling. Because, for the circuit shown.

 


Fig. 1.35 Stiff coupling network

For the circuit, shown above, in the mid frequency range,  $X_c$  is negligible.

$$\therefore i = \frac{V_{in}}{(R_S + R_L)}$$

$$V_{out} = i \cdot R_L = \left( \frac{V_{in}}{R_S + R_L} \right) R_L$$

$\therefore A_{(mid)} =$  Voltage gain in the mid frequency range is,

$$A_{mid} = \frac{V_{out}}{V_{in}} = \frac{R_L}{R_S + R_L}$$

For the complete circuit, 
$$\frac{V_{out}}{V_{in}} = \frac{R_L}{\sqrt{(R_S + R_L)^2 + X_c^2}}$$

When 
$$(R_S + R_L) = X_c = \frac{1}{2\pi f_c C}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_L}{\sqrt{2}(R_S + R_L)}$$

$$= 0.707 A_{mid}$$

$$\therefore f_c = \frac{1}{2\pi(R_S + R_L) \cdot C}$$

When 
$$X_c = 0.1 (R_S + R_L),$$

$$\frac{V_{out}}{V_{in}} = \frac{R_L}{\sqrt{(R_S + R_L)^2 + [0.1(R_S + R_L)]^2}}$$

$$\frac{V_{out}}{V_{in}} = 0.995 A_{mid}$$

$X_c$  is made =  $0.1(R_S + R_L)$ , at the lowest frequency. ( $f_c$  lower)

$\therefore$  At the frequency,  $A = 0.995 A_{mid}$ . So it is called as *Stiff Coupling*.

$$A = \frac{V_{out}}{V_{in}} = \frac{X_c}{\sqrt{R^2 + X_c^2}} = \frac{1}{\sqrt{1 + \left(\frac{R}{X_c}\right)^2}}$$

$$\therefore \frac{R}{X_c} = \frac{R}{\frac{1}{2\pi f_c}} = 2\pi f_c R = \frac{f}{f_c}$$

$$\therefore f_c = \frac{1}{2\pi RC}$$

$$\therefore A = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$$\text{Decibel voltage gain } A' = 20 \log \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$f_c$  = cutoff frequency.

$$\text{When } \frac{f}{f_c} = 0.1,$$

$$A' = 20 \log \frac{1}{\sqrt{1 + (0.1)^2}} \cong 0 \text{ db}$$

$$\text{When } \frac{f}{f_c} = 1,$$

$$A' = 20 \log \frac{1}{\sqrt{1 + 1^2}} = -3.01 \text{ db} \cong -3 \text{ db}$$

$$\text{When } \frac{f}{f_c} = 10,$$



$$A' = 20 \log \frac{1}{\sqrt{1+10^2}} = -20 \text{ db}$$

When  $\frac{f}{f_c} = 100,$

$$A' = 20 \log \frac{1}{\sqrt{1+100^2}} = -40 \text{ db}$$

When  $\frac{f}{f_c} = 1000,$


$$A' = 20 \log \frac{1}{\sqrt{1+1000^2}} = -60 \text{ db}$$

$\therefore$  when  $f = \frac{f_c}{10}, \quad A' = 0$

$$f = f_c, \quad A' = -3 \text{ db}$$

$$f = 10 f_c, \quad A' = -20 \text{ db}$$

and so on.

 


**Fig. 1.36 Frequency roll-off**

$\therefore$  A change of **20db** per decade change in frequency.

An Octave is a factor of 2 in frequency change

When  $f$  changes from 100 to 200 Hzs, it has changed by one octave.

When,  $f$  changes from 100 to 400 Hzs, it is two octaves for lead network, Bode Plot is

 

**Fig. 1.37 Variation of  $A_v$  with  $f$**

### 1.5 DESIGN OF SINGLE STAGE AMPLIFIERS

To form transistor amplifier configuration, we connect a load impedance  $Z_L$  and a signal source as shown in Fig. 1.38.

 


Fig 1.38 Amplifier circuit

$V_s$  is the signal source,  $R_s$  is the resistance of the signal source, and  $Z_L$  is the load impedance. Transistor can be connected in C.E, C.B. and C.C. Configuration. To analyse these circuits i.e. to determine the current gain  $A_i$ , Voltage gain  $A_v$ , input impedance, output impedance etc, we can use the  $h$  parameters. So the equivalent circuit for the above transistor amplifier circuit in general form without indicating C.E, C.B, or C.C. Configuration, can be denoted as in the Fig. 1.39.

 


Fig 1.39  $h$ -parameter equivalent circuit (general representation)

Current Amplification,

$$A_i = \frac{I_L}{I_1};$$

But  $I_L = -I_2$

$$\therefore A_i = -\frac{I_2}{I_1};$$

Negative sign is because  $I_2$  is always represented as flowing into the current source. For a transistor PNP or NPN type, if it is flowing out of the transistor,  $I_2$  is represented as  $-I_2$ . Now voltage across  $Z_L$  is taken with 2 as +ve and 2' as -ve. The directions of  $I_L$  are as shown and  $I_L = -I_2$ .

From the above circuit we have,

$$I_2 = h_f I_1 + h_o V_2$$

But  $V_2 = I_L Z_L = -I_2 Z_L$  (Since  $I_L = -I_2$ )

$$\begin{aligned}
 &\therefore I_2 = h_f I_1 - h_o \cdot Z_L \cdot I_2 \\
 \text{or} & I_2 + h_o Z_L I_2 = h_f I_1 \\
 & I_2 (1 + h_o Z_L) = h_f I_1 \\
 &\therefore \boxed{A_1 = - \frac{I_2}{I_1} = \frac{-h_f}{1 + h_o Z_L}} \dots\dots\dots ( 1.13 )
 \end{aligned}$$

Negative sign indicates that  $I_1$  and  $I_2$  are out of phase by  $180^\circ$ .

**1.5.1 INPUT IMPEDANCE ( $Z_i$ )**

Input impedance of any circuit is the impedance we measure looking back into the amplifier circuit. Now amplifier terminals are 1 and  $1'$ .  $R_s$  is the resistance of the signal source. So to determine the output  $z$  of the amplification alone, it need not be considered.

$$\begin{aligned}
 &Z_i = \frac{V_1}{I_1} \\
 \text{But} & V_1 = h_i I_1 + h_r V_2. \\
 \text{Hence} & Z_i = \frac{V_1}{I_1} = h_i + h_r \frac{V_2}{I_1} \dots\dots\dots ( 1.14 )
 \end{aligned}$$

$$\text{But } V_2 = -I_2 \cdot Z_L, \quad \therefore \frac{V_2}{I_1} = \left( \frac{-I_2}{I_1} \right) Z_L = A_1 Z_L \dots\dots\dots ( 1.15 )$$

Substituting the values of  $V_2$  in Equation ( 1.15 ),

$$\begin{aligned}
 &\boxed{Z_i = h_i + h_r \cdot A_1 \cdot Z_L} \\
 \text{But} & A_1 = \frac{-h_f}{1 + h_o Z_L} \\
 &\therefore Z_i = h_i - \frac{h_f h_r Z_L}{1 + h_o Z_L} \\
 &= h_i - \frac{h_f h_r}{\frac{1}{Z_L} + h_o} \\
 &\boxed{Z_i = h_i - \frac{h_f h_r}{Y_L + h_o}} \dots\dots\dots ( 1.16 )
 \end{aligned}$$

$Y_L$  is load admittance. Therefore, Input impedance is a function of load impedance. If  $Z_L = 0, Y_L = \infty,$

$$\therefore Z_i = h_i$$

**1.5.2 VOLTAGE GAIN ( $A_v$ )**

$$\begin{aligned}
 &A_v = \frac{V_2}{V_1} \\
 \text{But} & V_2 = +I_L \cdot Z_L = -I_2 \cdot Z_L \quad \text{Since, } I_2 = -I_L
 \end{aligned}$$

$$\begin{aligned} \text{But} \quad & I_2 = -A_1 \cdot I_1 \\ \therefore \quad & V_2 = +A_1 \cdot I_1 \cdot Z_L \\ & \frac{v_2}{v_1} = \frac{A_1 I_1 Z_L}{V_1} \end{aligned}$$

$$\begin{aligned} \text{But} \quad & \frac{V_1}{I_1} = Z_i \\ & z_i = h_i - \frac{h_f \cdot h_r}{\frac{1}{R_L} + h_o} \end{aligned}$$

$$\therefore A_V = \frac{A_1 Z_L}{Z_i}$$

$$\boxed{A_V = -\frac{-h_f z_L}{h_i + z_L (h_i h_o - h_f h_r)}} \quad \dots\dots\dots (1.17)$$

### 1.5.3 OUTPUT ADMITTANCE ( $Y_o$ )

The output impedance can be determined by using two assumptions  $Z_L = \infty$ , and  $V_s = 0$

$Y_o$  is defined as  $\frac{I_2}{V_2}$  with  $Z_L = \infty$

$$\text{But} \quad I_2 = h_f I_1 + h_o v_2.$$

Dividing by  $V_2$ ,

$$\frac{I_2}{V_2} = Y_o = \frac{h_f I_1}{V_2} + h_o. \quad \dots\dots\dots (1.18)$$

From the equivalent circuit with  $V_s = 0$ ,

$$R_s \cdot I_1 + h_i I_1 + h_r V_2 = 0.$$

Dividing by  $V_2$  Through out, we get

$$\frac{R_s \cdot I_1}{V_2} + \frac{h_i I_1}{V_2} + h_r = 0$$

$$\text{or} \quad \frac{I_1}{V_2} = \frac{-h_r}{h_i + R_s} \quad \dots\dots\dots (1.19)$$

Substitute this value in the equation for  $Y_o$

$$Y_o = h_f \left( \frac{-h_r}{h_i + R_s} \right) + h_o$$

$$\boxed{Y_o = h_o - \frac{h_f \cdot h_r}{h_i + R_s}}$$

Therefore,  $Z_o = 1/Y_o$

Therefore, output admittance is a function of Source Resistance  $R_s$  where as  $Z_i$  is a function of  $Y_L$ . If  $R_s = 0$ ,  $Y_o \cong h_o$ . Since  $(h_r h_i/h_o)$  is very small.

**1.5.4 VOLTAGE GAIN ( $A_{vs}$ ) CONSIDERING SOURCE RESISTANCE ( $R_s$ )**

$$\therefore A_{vs} = \frac{V_2}{V_s} = \frac{V_2}{V_1} \times \frac{V_1}{V_s} = A_v \cdot \frac{V_1}{V_s}$$

This is the equivalent circuit of the input side of the amplifier circuit. (Fig. 1.40).

$$\therefore V_1 = \frac{V_s \cdot Z_i}{Z_i + R_s}$$

$$\therefore A_{vs} = \frac{A_v \cdot Z_i}{Z_i + R_s}$$

$$A_v = \frac{v_2}{v_1}$$

$$\therefore A_v \cdot Z_i = \frac{V_2}{V_1} \cdot Z_i$$

But  $V_2 = I_L \cdot Z_L$ ;  $V_1 = I_1 \cdot Z_i$

$$\therefore A_v \cdot Z_i = \frac{I_L \cdot Z_L \cdot Z_i}{I_1 \cdot Z_L} = A_T \cdot Z_L$$

$$\therefore \boxed{A_{vs} = \frac{A_T \cdot Z_L}{R_s + Z_i}} \quad \text{If } R_s = 0, A_{vs} = A_v \quad \dots\dots\dots (1.20)$$

Hence  $A_v$  is the voltage gain of an ideal voltage source with zero terminal resistance.

**1.5.5 CURRENT GAIN ( $A_{is}$ ) CONSIDERING SOURCE RESISTANCE ( $R_s$ )**

The input source can also be represented as a current source  $I_s$  in parallel with resistance  $R_s$  or voltage source  $V_s$  in series with resistance  $R_s$ . Now let us consider the input source as a current source in parallel with  $R_s$ . The equivalent circuit is (Fig. 1.41)

$$A_{is} = \frac{I_L}{I_s}; I_L = -I_2$$

$$\therefore A_{is} = \frac{I_L}{I_s} = -\frac{I_2}{I_s}$$

$$A_{is} = -\frac{I_2}{I_s} = -\frac{I_2}{I_1} \cdot \frac{I_1}{I_s}$$

$$= A_T \cdot \frac{I_1}{I_s}$$

$$\therefore A_T = \frac{-I_2}{I_1}$$

 


Fig 1.40 Voltage source.

 


Fig 1.41 Current source

$\dots\dots\dots (1.21)$

From the Fig 6.27,  $I_1 = \frac{I_s \cdot R_s}{R_s + Z_i}$

$$\therefore A_{IS} = \frac{A_I \times R_s}{(R_s + Z_i)} = \frac{A_I \cdot R_s}{(R_s + Z_i)}$$

If  $R_s = \infty$ ,  $A_I = A_{IS}$ . Therefore,  $A_I$  is the current gain for an ideal source

Now 
$$A_{VS} = \frac{A_I \cdot Z_L}{Z_i + R_s} \quad \dots\dots\dots (1.22)$$

$$A_{IS} = \frac{A_I \cdot R_s}{Z_i + R_s} \quad \dots\dots\dots (1.23)$$

Dividing (1.10) and (1.11),  $\frac{A_{VS}}{A_{IS}} = \frac{Z_L}{R_s}$ .

or 
$$A_{VS} = A_{IS} \cdot \frac{Z_L}{R_s} \quad \dots\dots\dots (1.24)$$

This equation is independent of the transistor parameters This is valid if the equivalent current and voltage sources have the same resistance.

### 1.5.6 POWER GAIN ( $A_P$ )

$$A_P = \frac{P_2}{P_1} = \frac{V_2 I_L}{V_1 I_1}$$

$$= A_V \cdot A_I$$

$$\therefore A_V = \frac{A_I \cdot Z_L}{Z_i},$$

$$\therefore A_P = \frac{A_I^2 Z_L}{Z_i} \quad \dots\dots\dots (1.25)$$

### COMPARISON OF THE CE, CB, CC CONFIGURATIONS

**C.E :** Of the three, it is the most versatile. Its voltage and current gain are  $> 1$ . Input and output resistance vary least with  $R_s$  and  $R_L$ .  $R_i$  and  $R_o$  values lie between maximum and minimum for all the three configurations. Phase shift of  $180^\circ$  between  $V_i$  and  $V_o$ . Power Gain is Maximum.

**C.B :**  $A_I < 1$   $A_V > 1$ .  $R_i$  is the lowest and  $R_o$  is the highest. It has few applications. Sometimes it is used to match low impedance source  $V_i$  and  $V_o$ . No phase shift.

**C.C :**  $A_V < 1$ .  $A_I$  is very high. It has very **high input Z and low output Z**. **So it is used as a buffer** between high Z source and low impedance load. It is also called as **emitter follower**.

To analyse circuit consisting of a number of Transistors, each Transistor should be replaced by its equivalent circuit in h-parameters. The emitter base and collector points are indicated and other circuit elements are connected without altering the circuit Configuration. This way the circuit analysis becomes easy.

**Example 1.7**

Find the Common Emitter Hybrid parameters in terms of the Common Collector Hybrid parameters for a given transistor.

**Solution**

We have to find  $h_{ie}$ ,  $h_{re}$ ,  $h_{fe}$  and  $h_{oe}$  in terms of  $h_{ic}$ ,  $h_{rc}$ ,  $h_{fc}$  and  $h_{oc}$ .

The transistor circuit in Common Collector Configuration is shown in Fig. 1.42. The h-parameter equivalent circuit is shown in Fig. 1.43.

 


Fig 1.42 For example 1.7

 


Fig 1.43 Equivalent circuit

C.C :

$$v_b = h_{ic} \cdot i_b + h_{rc} v_e$$

$$i_e = h_{fc} i_b + h_{oc} v_e$$

$$i_c = h_{fc} i_b - i_e$$

$$= (h_{fc} i_b - h_{oc} v_e)$$

$$v_{be} = i_b \cdot h_{ic} - h_{rc} v_{ce} + v_{ce} = i_b \cdot h_{ic}$$

Since  $v_{ce} = 0$

But 
$$h_{ie} = \left. \frac{V_{be}}{I_b} \right|_{V_{ce}=0}$$

$\therefore$   $h_{ie} = h_{ic}$  ..... ( 1.26 )

$$h_{re} = \left. \frac{i_c}{i_b} \right|_{V_{ce} = 0}$$

$$i_c = -i_b - i_e = -i_b - h_{fc} \cdot i_b + h_{oc} v_{ce}$$

But

$$\begin{aligned}
 v_{ce} &= 0 \\
 &= -i_b - (h_{fc} i_b - h_{oc} v_{ce}) \\
 &= -i_b - h_{fc} i_b + h_{oc} v_{ce} \quad v_{ce} = 0
 \end{aligned}$$

$$h_{fe} = \frac{-i_b - h_{fc} i_b}{i_b} = -(1 + h_{fc})$$

$$\boxed{h_{fe} = -(1 + h_{fc})} \quad \text{..... ( 1.27 )}$$

$$h_{re} = \left. \frac{V_{be}}{V_{ce}} \right|_{i_b=0}$$

$$V_{be} = i_b h_{ie} - h_{rc} V_{ce} + V_{ce}$$

$$i_b = 0$$

$$\therefore h_{re} = - \frac{h_{rc} V_{ce} + V_{ce}}{V_{ce}} = 1 - h_{rc}$$

$$\boxed{h_{re} = 1 - h_{rc}} \quad \text{..... ( 1.28 )}$$

$$h_{oe} = \left. \frac{i_c}{V_{ce}} \right|_{i_b=0}$$

$$i_c = -i_e - i_b$$

$$\text{But } i_b = 0.$$

$$i_c = -i_e$$

$$i_e = V_{ce} h_{oc}$$

$$\therefore \frac{i_c}{V_{ce}} = \frac{-i_e}{V_{ce}} = -h_{oc}$$

$$\therefore i_c = -i_e = -h_{oc} V_{ce}$$

$$\therefore \boxed{h_{oe} = -h_{oc}} \quad \text{..... ( 1.29 )}$$

Since,

$$i_b = 0$$

$$\therefore i_c = V_{ce} \times h_{oc}$$

$$\therefore h_{oe} = h_{oc} \quad \text{is admittance in mhos } (\Omega).$$



### 1.6 HIGH INPUT RESISTANCE TRANSISTOR CIRCUITS

In some applications the amplifier circuit will have to have very high input impedance. Common Collector Amplifier circuit has high input impedance and low output impedance. But its  $A_V < 1$ . If the input impedance of the amplifier circuit is to be only 500 k $\Omega$  or less the Common Collector Configuration can be used. This circuit is known as the *Darlington Connection* (named after Darlington) or *Darlington Pair Circuit*. (Fig. 1.44).

 


Fig 1.44 Darlington pair circuit.

In this circuit, the two transistors are in Common Collector Configuration. The output of the first transistor  $Q_1$  (taken from the emitter of the  $Q_1$ ) is the input to the second transistor  $Q_2$  at the base. The input resistance of the second transistor constitutes the emitter load of the first transistor. So, Darlington Circuit is nothing but two transistors in Common Collector Configuration connected in series. The same circuit can be redrawn as AC equivalent circuit. So, DC is taken as ground shown in Fig.1.45. Hence, 'C' at ground potential. Collectors of transistors  $Q_1$  and  $Q_2$  are at ground potential. The AC equivalent Circuit is shown in Fig. 1.45.

There is no resistor connected between the emitter of  $Q_1$  and ground i.e., Collector Point. So, we can assume that infinite resistance is connected between emitter and collector. For the analysis of the circuit, consider the equivalent circuit shown in Fig. 1.45 and we use Common Emitter *h-parameters*,  $h_{ie}$ ,  $h_{re}$ ,  $h_{oe}$  and  $h_{fe}$ .

For PNP transistor,  $I_c$  leaves the transistor,  $I_e$  enters the transistor and  $I_b$  leaves the transistor.

 


Fig 1.45 Equivalent circuit.

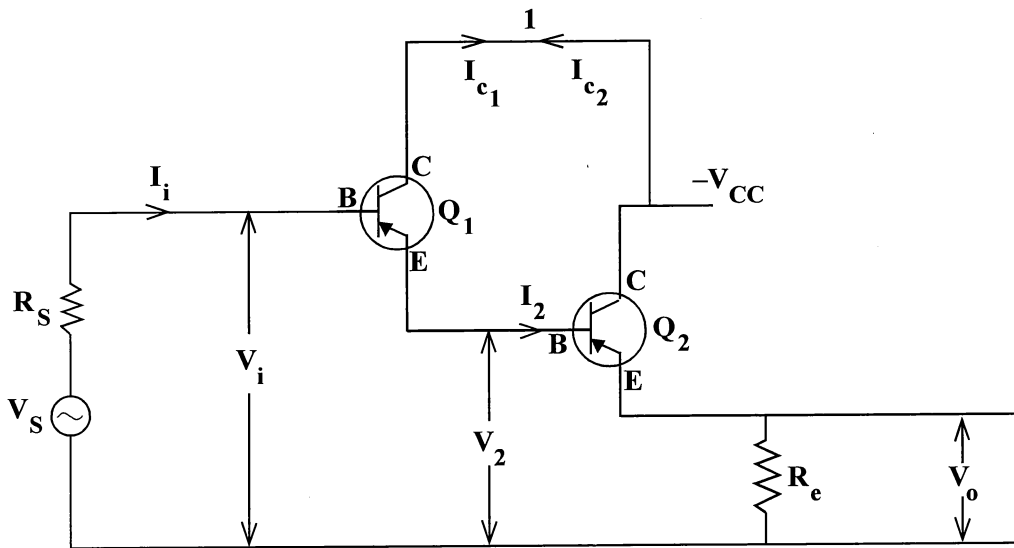


Fig 1.46 Darlington pair circuit.

1.6.1 CURRENT AMPLIFICATION FOR DARLINGTON PAIR

$$\begin{aligned}
 I_c &= I_{c1} + I_{c2} \\
 I_{c1} &= I_{b1} h_{fe} \\
 I_{c2} &= I_{b2} h_{fe} \text{ (Assuming identical transistor and } h_{fe} \text{ is same)} \\
 \text{But } I_{b2} &= I_{e1} \text{ (the emitter of } Q_1 \text{ is connected to the base of } Q_2) \\
 \therefore I_c &= I_{b1} h_{fe} + I_{e1} h_{fe} \quad \dots(1.30) \\
 I_{e1} &= I_{b1} + I_{c1} = I_{b1} (1 + h_{fe}) \quad \dots(1.31) \\
 \therefore I_{c1} &= h_{fe} I_{b1}
 \end{aligned}$$

Substituting equation (1.31) in (1.30),

$$I_c = I_{b_1} h_{fe} + I_{b_1} (1 + h_{fe}) h_{fe} = I_{b_1} (2h_{fe} + h_{fe}^2)$$

But  $h_{fe}^2 \gg 2h_{fe}$

Since,  $h_{fe}$  is of the order of 100.

$$\therefore I_c = I_{b_1} h_{fe}^2$$

It means that we get very large current amplification  $\left( A_I = \frac{I_c}{I_{b_1}} \right)$  in the case of Darlington

Pair Circuit, it is of the order  $h_{fe}^2$  i.e.  $100^2 = 10,000$ .

$$\therefore \boxed{A_I = \frac{I_c}{I_{b_1}} \cong (h_{fe})^2}$$

### 1.6.2 INPUT RESISTANCE ( $R_i$ )

Input resistance  $R_{i_2}$  of the transistor  $Q_2$  (which is in Common Collector Configuration) in terms of *h-parameters* in Common Emitter Configuration is,

$$R_{i_2} = h_{ie} + (1+h_{fe}) R_L$$

But  $h_{ie} \ll h_{fe} R_L$ , and  $h_{fe} R_E \gg h_{ie} A_{I_2} = \frac{I_0}{I_2} = (1 + h_{fe})$

Here  $R_L$  is  $R_e$ , since, output is taken across emitter resistance.

$$\therefore R_{i_2} \cong (1 + h_{fe}) R_e$$

The input resistance  $R_{i_1}$  of the transistor  $Q_1$  is, since it is in Common Collector Configuration,

$$R_{i_1} = h_{ic} + h_{rc} A_I R_L$$

Expressing this in term of Common Emitter *h-parameters*,

$$h_{ic} \cong h_{ie}; h_{rc} \cong 1.$$

(For Common Collector Reverse Voltage Gain = 1) and  $R_L$  for transistor  $Q_1$  is the input resistance of transistor  $Q_2$ .

$$\therefore R_{i_1} = h_{ie} + A_{I_1} R_{i_2}. R_{i_2} \text{ is large,}$$

Therefore,  $h_{oe} R_{i_2} \leq 0.1$ . and  $A_I \neq 1 + h_{fe}$

$$\begin{aligned} R_{i_1} &\cong A_{I_1} R_{i_2} \\ R_{i_2} &= (1 + h_{fe}) R_e \end{aligned}$$

But the expression for Common Collector Configuration in terms of Common Emitter *h-parameters* is

$$A_I = \frac{1 + h_{fe}}{1 + h_{oe} R_L}$$

Here,  $R_L = R_{i_2}$  and  $R_{i_2} = (1 + h_{fe}) R_e$ .

$$\therefore A_{I1} = \frac{1 + h_{fe}}{1 + h_{oe} (1 + h_{fe}) R_e}$$

$h_{oe} R_e$  will be  $< 0.1$  and can be neglected.

$$\therefore h_{oe} \text{ value is of the order of } \mu \text{ mhos (micro mhos)}$$

$$\therefore A_{I1} = \frac{1 + h_{fe}}{1 + h_{oe} h_{fe} R_e}$$

$$\therefore R_{i1} \approx A_{I1} \cdot R_{i2}$$

$$R_i \approx \frac{(1 + h_{fe})^2 R_e}{1 + h_{oe} h_{fe} R_e}$$

This is a very high value. If we take typical values, of  $R_e = 4 \text{ k}\Omega$ , using *h-parameters*,

$$R_{i2} = 205 \text{ k}\Omega.$$

$$R_i = 1.73 \text{ M}\Omega.$$

$$A_I = 427.$$

Therefore, Darlington Circuit has *very high input impedance* and very *large current gain* compared to Common Collector Configuration Circuit.

### 1.6.3 VOLTAGE GAIN ( $A_V$ )

General expression for  $A_V$  for Common Collector in term of *h-parameters* is

$$A_V = 1 - \frac{h_{ie}}{R_i}; \quad h_{ie} \cong h_{ic} \quad \text{or} \quad A_{V1} = \frac{V_2}{V_i} = \left[ \frac{1 - h_{ie}}{R_{i1}} \right]$$

$$\text{But} \quad R_i \cong A_{I1} \cdot R_{i2} \quad \therefore A_{V1} = \left( \frac{h_{ie}}{A_{I1} R_{i2}} \right)$$

$$\therefore A_{V2} = \frac{V_o}{V_2} = \left( 1 - \frac{h_{ie}}{R_{i2}} \right)$$

Therefore, over all Voltage Gain  $A_V = A_{V1} \times A_{V2}$

$$= \left( 1 - \frac{h_{ie}}{A_{I1} \cdot R_{i2}} \right) \left( 1 - \frac{h_{ie}}{R_{i2}} \right)$$

$$A_V \cong \left( 1 - \frac{h_{ie}}{R_{i2}} \right) \quad \because A_{I1} R_{i2} \gg h_{ie} \quad \because A_{I1} \text{ is } \gg 1$$

Therefore,  $A_V$  is always  $< 1$ .

### 1.6.4 OUTPUT RESISTANCE ( $R_o$ )

The general expression for  $R_o$  of a transistor in Common Collector Configuration in terms of Common Emitter *h-parameters* is,

$$R_o = \frac{R_s + h_{ie}}{1 + h_{fe}}$$

$$\therefore R_{o1} = \frac{R_s + h_{ie}}{1 + h_{fe}}$$

Now for the transistor  $Q_2$ ,  $R_s$  is  $R_{o1}$ .

$$\therefore R_{o2} = \frac{R_s + h_{ie}}{1 + h_{fe}} + h_{ie}$$

Therefore,  $R_{o2}$  is the output resistance of the Darlington Circuit.

$$\therefore R_{o2} = \frac{R_s + h_{ie}}{(1 + h_{fe})^2} + \frac{h_{ie}}{1 + h_{fe}}$$

This is a small value, since,  $1 + h_{fe}$  is  $\gg 1$ .

Therefore, the characteristic of Darlington Circuit are

1. *Very High Input Resistance ( of the order of  $M\Omega$  ).*
2. *Very Large Current Gain ( of the order of 10, 000 ).*
3. *Very Low Output Resistance ( of the order of few  $\Omega$  ).*
4. *Voltage Gain,  $A_v < 1$ .*

Darlington Pairs are available in a single package with just three leads, like one transistor in integrated form.

#### **Disadvantages :**

We have assumed that the ***h-parameters*** of both the transistor are identical. But in practice it is difficult to make out. ***h-parameters*** depend upon the operating point of  $Q_1$  and  $Q_2$ . Since the emitter current of transistor  $Q_1$  is the base current for transistor  $Q_2$ , the value of  $I_{c2} \gg I_{c1}$

1. *The quiescent or operating conditions of both the transistor will be different.  $h_{fe}$  value will be small for the transistor  $Q_1$ .  $\therefore h_{fe} = (I_c/I_b) \cdot I_{b2}$  is less*  
*CDIL make CIL997 is a transistor of Darlington Pair Configuration with  $h_{fe} = 1000$ .*

2. *The second drawback is leakage current of the 1<sup>st</sup> transistor  $Q_1$  which is amplified by the second transistor  $Q_2$  ( $\because I_{e1} = I_{b2}$ ).*

*Hence overall leakage current is more. Leakage Current is the current that flows in the circuit with no external bias voltages applied*

**(a)** *The ***h-parameters*** for both the transistors will not be the same.*

**(b)** *Leakage Current is more.*

**(b)** *Darlington transistor pairs in single package are available with  $h_{fe}$  as high as 30,000*

1.6.5 R-C COUPLED AMPLIFIER CIRCUIT (SINGLE STAGE)

 


Fig. 1.47 RC Coupled amplifier circuit

The circuit is shown in Fig. 1.47.

$R_L$  is the load resistor that develops the output voltage from the transistor.  $C_2$  is used to couple the AC component of the output to  $R_L$ . (Fig. 1.47).

In the self bias circuit,  $R_E$  the emitter resistors is connected between emitter and ground. But through  $R_E$ , a negative feedback path is there. So to prevent A.C. negative feedback, if a capacitor is connected in parallel with  $R_E$ , and it is chosen such that  $X_E$  provides least resistance path compared to  $R_E$ , AC signal passes through  $C_E$  and not through  $R_E$ . Therefore, there will not be any negative feedback for AC signals.

$$X_E \text{ is chosen such that } X_E \leq \frac{R_E}{10}$$

and  $X_E$  is chosen at the frequency  $f_1$ . For frequencies higher than  $f_1$ ,  $X_E$  any way will be less.

The equivalent circuit for the above transistor configuration is shown in Fig. 1.48.

 


Fig. 1.48 Equivalent circuit

Suppose the value of  $C_C$  is very large. Then at the low and medium frequencies, the impedance is negligible. So the *equivalent* circuit is as shown. We shall consider the effect of  $C_E$  later.

From the *equivalent* circuit,

$$V_0 = - h_{fe} \cdot i_b \cdot R_L$$

negative sign is used since it is NPN transistor. The collector current is flowing into the transistor.

Input current,  $I_b = V_s / R_s + R_i$

For a transistor amplifier circuit in common emitter configuration,

$$R_i = h_{ie} + (1 + h_{fe}) Z_E$$

Where  $Z_E = R_E$  in parallel with  $C_E = \frac{R_E}{1 + j\omega C_E R_E}$

$$\therefore V_0 = -h_{fe} \cdot R_L \times \frac{V_S}{R_S + h_{ie} + \frac{(1 + h_{fe})R_E}{1 + j\omega C_E R_E}}$$

$$\therefore A_V = \frac{V_0}{V_S}$$

$A_V$  at low frequencies, (LF)

$$A_V(LF) = \frac{V_0}{V_S}$$

$$A_V(LF) = \frac{-h_{fe} \cdot R_L}{R_S + h_{ie} + \frac{(1 + h_{fe})R_E}{1 + j\omega C_E R_E}}$$

When  $\omega$  is large,  $\frac{(1 + h_{fe})R_E}{1 + j\omega C_E R_E}$  can be neglected. So in the Mid Frequency range, (M.F.),

$$\therefore A_V(M.F) = \frac{-h_{fe} R_L}{R_S + h_{ie}}$$

In this expression, there is no  $f$  or  $\omega$  term. Hence in the mid frequency range,  $A_V$  is independent of  $f$  or the gain remains constant, irrespective of change in frequency.

### 1.6.6 EFFECT OF COUPLING CAPACITOR ON LOW FREQUENCY RESPONSE

Consider the circuit shown in Fig. 1.49

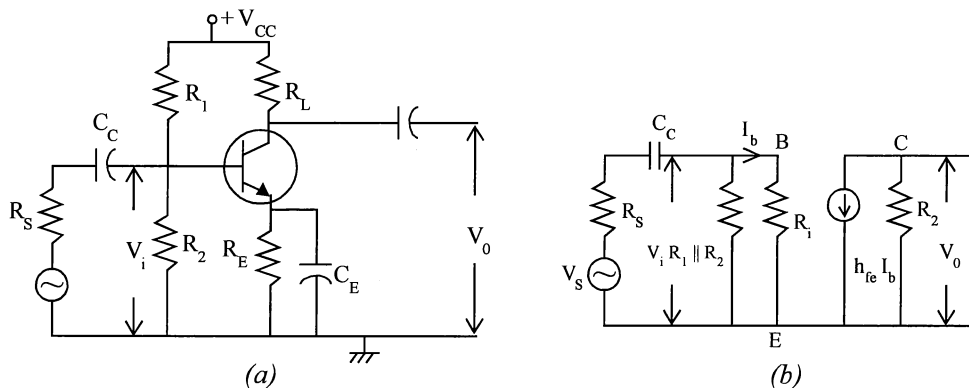


Fig. 1.49 Effect of coupling capacitors

Suppose that the value of  $C_E$  is such that its effect on the frequency response can be neglected and the value of  $X_C$  at low frequencies is such that it is not a simple short circuit for A.C. signals, so that its effect has to be considered.

The effect of  $C_E$  is, voltage drop across  $C_C$  will reduce  $V_i$  with a corresponding drop in  $V_0$ .

The frequency at which the gain drops by a factor of  $\frac{1}{\sqrt{2}}$ , is the lower 3 db frequency.

$$f_1 = \frac{1}{2\pi(R_S + R_i')C_C}$$

where  $R_i' = R_1 \parallel R_2 \parallel R_i$   
and  $R_i = h_{ie}$ , for an ideal capacitor  $C_E$ .

These expressions are valid when emitter is bypassed. In AC equivalent circuit, emitter is assumed to be at GND potential. Therefore  $C_E$  has no effect.

Large values of capacitors are required (10  $\mu$ F, 5  $\mu$ F etc.) in transistor amplifiers for coupling and bypass purposes for good low frequency response. Since these values are large, only electrolytic capacitors are used. Capacitors of such large values are not available in other types of capacitors. These capacitors are bulky. So audio amplifier circuits, Integrated Circuits (I.C) often have large capacitors connected externally to the (I.C) itself to provide the required low frequency response.

### Example : 1.8

In the Resistance Capacitance (RC) coupled amplifier,  $A_{vm} = 50$ ,  $f_1 = 50$  Hz and  $f_2 = 100$  kHz. Find the values of frequencies at which the gain reduces to 40 on either side of midband region.

**Solution :**

$$A_{vH} = \frac{A_{VMF}}{1 + j \left( \frac{f}{f_2} \right)}$$

$$\text{Phase shift angle } \phi = 180^\circ - \tan^{-1} \left( \frac{f}{f_2} \right)$$

$$A_{vLF} = \frac{A_{VMF}}{\sqrt{1 + \left( \frac{f_1}{f} \right)^2}}$$



$$A_{VL} = \frac{A_{VM}}{1 + j \left( \frac{f_1}{f} \right)}$$

$$\phi = 180^\circ + \tan^{-1} \left( \frac{f_1}{f} \right)$$

At the frequency  $f$ , the gain is  $A_{VLF} = 40$ .

$$A_{VLF} = 40, \quad A_{VM.F} = 50, \quad f_1 = 50 \text{ Hzs}, f = ?$$

$$\frac{40}{50} = \frac{1}{\sqrt{1 + \left( \frac{50}{f} \right)^2}} \quad \therefore f = 66.66 \text{ Hz.}$$

$$A_{VHF} = \frac{A_{VM.F}}{\sqrt{1 + \left( \frac{f}{f_2} \right)^2}}$$

At frequency  $f$ ,  $A_{VHF} = 40$ .  $\therefore f = ?$   $f_2 = 100 \text{ kHz}$ .

$$\frac{40}{50} = \frac{1}{\sqrt{1 + \left( \frac{f}{100 \times 10^3} \right)^2}}; \quad f = 75 \text{ kHz.}$$

### Example : 1.9

An amplifier of 40db gain has both its input and output load resistances equal to  $600\Omega$ . If the amplifier input power is  $-30\text{db}$ , what is the output power and voltage? Assume that reference power level used is  $1\text{mW}$  in a  $600\Omega$  resistance.

#### Solution :

Since it is logarithmic scale, for db,

$$P_0 \text{ (db)} = (P_i)_{\text{db}} + (\text{gain}_{\text{db}});$$

$$P_0 = P_i \times A_P \quad \text{Output power } (P_0) = \text{Input Power } (P_i) \times \text{Power Gain } (A_P)$$

$$P_0 = ? P_i = -30\text{db}, \text{ gain} = 40\text{db}$$

$$\therefore P_0 = -30 + 40 = \mathbf{10\text{db.}}$$

Reference power level =  $1 \text{ mW}$ .

$$\therefore 10 \log = \left( \frac{P_0}{1\text{mW}} \right) = 10\text{db}$$

$$10 \log \frac{P_0}{0.001} = 10$$

$$\log \frac{P_0}{0.001} = 1$$

$$\frac{P_0}{0.001} = 10$$

$$\therefore \log 10 = 1$$

$$\begin{aligned} \therefore P_0 &= 10 \times 0.001 \\ &= \mathbf{10\text{mW}} \end{aligned}$$

(With respect to, 1mW, the input and output powers are compared and expressed in db.)

$$\therefore 10 \log \frac{P_0}{1\text{mW}} = 10\text{db}$$

RMS output voltage is,

$$P_0 = \frac{V_0^2}{R}$$

$$\begin{aligned} \text{or } V_0 &= \sqrt{P_0 \cdot R} = \sqrt{10 \times 10^{-3} \times 600} \\ &= \sqrt{6} = \mathbf{2.45\text{ V}} \end{aligned}$$

### Example : 1.10

An amplifier has  $R_i = 0.5\text{ k}\Omega$  and  $R_o = 0.05\text{ k}\Omega$ . The amplifier gives an output voltage of 1V peak for an input voltage of 1mV peak. Find  $A_v$ ,  $A_p$ ,  $A_p$  in db.

**Solution :**

$$V_0 (\text{peak}) = 1\text{V.}$$

$$V_{0(\text{rms})} = \frac{V_0(\text{peak})}{\sqrt{2}}; \quad V_{0(\text{rms})} = \frac{1\text{V}}{\sqrt{2}}$$

$$A_v = 20 \log \left( \frac{V_0}{V_i} \right)$$

$$= 20 \log \left( \frac{1}{1\text{mV}} \right) = 60 \text{ db}$$

$$\begin{aligned} I_{i(\text{peak})} &= V_{i(\text{Peak})} / R_i \\ &= 1\text{mV}/500 \\ &= 2 \times 10^{-6} \text{ A.} \end{aligned}$$

$$\begin{aligned} I_{0(\text{peak})} &= V_{0(\text{Peak})} / R_0 \\ &= 1/50 \\ I_{0(\text{Peak})} &= 0.02 \text{ A.} \end{aligned}$$

$$\therefore \text{Current Gain } (A_i) = 20 \log \left( \frac{0.02}{2 \times 10^{-6}} \right) = 80 \text{ db}$$

$$P_i = \frac{V_i^2}{R_i} = 10^{-9} \text{ W;}$$

$$P_0 = \frac{V_0^2}{R_0} = 10^{-2} \text{ W.}$$

$$\text{Power gain, } A_p = 10 \log \left( \frac{P_0}{P_i} \right) = 70 \text{ db}$$

### SUMMARY

- Electronic amplifiers are classified based on (a) Frequency range (b) Type of coupling (c) Output power (d) Type of signal handled.
- Power amplifiers are classified as (a) Class A (b) Class B (c) Class AB (d) Class C (e) Class D and (f) Class S amplifiers.
- The type of distortion that can occur are classified as (a) amplitude (b) frequency (c) Phase distortions
- h-parameter analysis enables to derive expressions for  $A_v$ ,  $R_i$ ,  $R_o$ ,  $A_p$  of amplifiers in terms of transistor parameters and circuit components. These equations are derived.
- Gain is expressed in decibels.
- Comparison between the three types, C.E, CB, CC amplifiers is given and expressions are derived for  $A_v$ ,  $Z_i$ ,  $Z_o$ ,  $A_p$  etc.
- Darlington pair amplifier circuit gives high  $R_i$  ( $M\Omega$ ) large current gain (10K), low voltage gain ( $<1$ ) and low  $R_o$  (few  $\Omega$ ). The circuit is explained and equations are derived.
- Single stage R-C coupled amplifier circuit is given and expressions for lower cut-off frequency and upper cut-off frequency are given.

### OBJECTIVE TYPE QUESTIONS

1. The units of h-parameters are .....
2. h-parameters are named as hybrid parameters because .....
3. The general equations governing h-parameters are
 
$$V_1 = \dots\dots\dots$$

$$I_2 = \dots\dots\dots$$
4. The parameter  $h_{re}$  is defined as  $h_{re} = \dots\dots\dots$
5. h-parameters are valid in the ..... frequency range.
6. Typical values of h-parameters in Common Emitter Configuration are .....
7. The units of the parameter  $h_{rc}$  are .....
8. Conversion Efficiency of an amplifier circuit is .....
9. Expression for current gain  $A_I$  in terms of  $h_{fe}$  and  $h_{re}$  are  $A_I = \dots\dots\dots$
10. In Common Collector Configuration, the values of  $h_{rc} \simeq \dots\dots\dots$
11. In the case of transistor in Common Emitter Configuration, as  $R_L$  increases,  $R_i \dots\dots\dots$
12. Current Gain  $A_I$  of BJT in Common Emitter Configuration is high when  $R_L$  is .....
13. Power Gain of Common Emitter Transistor amplifier is .....
14. Current Gain  $A_I$  in Common Base Configuration is .....
15. Among the three transistor amplifier configurations, large output resistance is in ..... configuration.
16. Highest current gain, under identical conditions is obtained in ..... transistor amplifier configuration.
17. C.C Configuration is also known as ..... circuit.

**ESSAY TYPE QUESTIONS**

1. Write the general equations in terms of h-parameters for a BJT in Common Base Amplifiers configuration and define the h-parameters.
2. Convert the h-parameters in Common Base Configuration to Common Emitter Configuration, deriving the necessary equations.
3. Compare the transistor (BJT) amplifiers circuits in the three configurations with the help of h-parameters values.
4. Draw the h-parameter equivalent circuits for Transistor amplifiers in the three configurations.
5. With the help of necessary equations, discuss the variations of  $A_v$ ,  $A_p$ ,  $R_i$ ,  $R_o$ ,  $A_p$  with  $R_s$  and  $R_L$  in Common Emitter Configuration.
6. Discuss the Transistor Amplifier characteristics in Common Base Configuration and their variation with  $R_s$  and  $R_L$  with the help of equations.
7. Compare the characteristics of Transistor Amplifiers in the three configurations.

## ANSWERS OF OBJECTIVE TYPE QUESTIONS

1.  $\Omega$ , mhos and constants
2. the units of different parameters are not the same
3. 
$$\begin{matrix} h_{11}I_1 + h_{12}V_2 \\ h_{21}I_1 + h_{22}V_2 \end{matrix}$$
4. 
$$\left. \frac{\partial V_B}{\partial V_C} \right|_{I_B=K}$$
5. Audio
6. 
$$\begin{matrix} h_{ie} = 1 \text{ k}\Omega, h_{re} = 1.5 \times 10^{-4}, \\ h_{oe} = 6 \mu\text{mhos}, h_{fe} = 200 \end{matrix}$$
7. No units (constant)
8. 
$$\frac{\text{AC Signal Power Delivered to the Load}}{\text{DC Input Power}} \times 100$$
9. 
$$\frac{h_{fe}}{1 + h_{oe}R_L}$$
10. 1
11. Decreases
12. Low
13. Large
14.  $< 1$
15. Common Base configuration
16. Common Collector Configuration
17. Voltage follower/buffer