

Contents

CHAPTER 1

D.C. CIRCUIT CONCEPTS AND CIRCUIT ELEMENTS

D.C. CIRCUIT CONCEPTS AND CIRCUIT ELEMENTS - I

1.1	Introduction to basics of Electrical Engineering	1
1.1.1	Circuit Concepts - Concepts of Networks	1
1.2	Current Flow	2
1.2.1	Potential and Potential Difference	2
1.2.2	Electric Current	3
1.3	Active and Passive Elements	4
1.3.1	Sources of Electrical Energy - Voltage Source	4
1.3.2	Sources of Electrical Energy - Current Source	5
1.3.3	D.C. & A.C. Sources	6
1.3.4	Unilateral and Bilateral Elements	8
1.3.5	Effect of Temperature on Resistance	11
1.3.6	Electrical Conductance	12
1.4	V-I Relationship for Resistance—Ohm's Law.....	13
1.4.1	Linear & Non-Linear Resistances	15

1.5 Electrical Power.....	16
1.6 Energy Calculations	18
1.7 Electrical Energy	18
1.8 Kirchoff's Laws.....	19
1.8.1 Kirchoff's Voltage Law (KVL)	19
1.8.2 Kirchoff's Current Law (KCL or KIL)	20
1.9 Resistances in Series.....	25
1.10 Resistances in Parallel	29
1.10.1 Division of Currents in Parallel Circuits	31
1.11 Series-Parallel Resistances	35
1.12 Resistances in Star or Delta Connections	40
1.12.1 The Equivalent Star Resistances for given Delta Connected Resistances	40
1.12.2 The Equivalent Delta Resistances for given Star Connected Resistances	42
1.13 Uses of Resistance	48

D.C. CIRCUIT CONCEPTS AND CIRCUIT ELEMENTS - II

1.14 Introduction to Energy Storing Elements	49
1.15 Capacitance Parameter.....	49
1.15.1 V-I Relationship for Capacitor–The Current Flowing through a Capacitor	51
1.15.2 Energy Stored in a Charged Capacitance	53
1.15.3 Parallel Plate Capacitor with Guard Ring	58
1.15.4 Capacitances in Series or Series Capacitors	58
1.15.5 Capacitances in Parallel or Parallel Capacitors	64
1.15.6 Capacitances in Series-Parallel	68
1.15.7 Dielectric Strength and Breakdown	70
1.15.8 Electrostatic Induction	71
1.15.9 Uses of Capacitors.....	71

1.16 Inductance	71
1.16.1 Magnetic Field of a Solenoid	72
1.16.2 Self Inductance of a Coil	74
1.16.3 Voltage Drop across the Inductance	77
1.16.4 Energy Stored in an Inductor or Coil or Inductance	78
1.16.5 Inductances in Series or Series Inductors without Mutual Induction	82
1.16.6 Inductances in Parallel or Parallel Inductors without Mutual Induction ..	83
1.16.7 Inductances in Series-Parallel without Mutual Induction	84
1.16.8 Mutual Induction between Coils	85
1.16.9 Dot Convention for Mutual Inductances	88
1.16.10 Expression for Mutual Inductance M in Terms of Dimensions of Two Coils	91
1.16.11 Coefficient of Magnetic Coupling or Magnetic Coupling between two Coils	91
1.16.12 Variable Inductance	95
1.16.13 Magnetic Hum	95
1.17 Uses of Inductors	95
Comprehension - 1	97
Exercise - 1	103

CHAPTER 2

D.C. CIRCUIT ANALYSIS

2.1 Introduction	113
2.1.1 Controlled or Dependent Voltage and Current Sources	114
2.1.2 Controlled Source or Dependent Source	114
2.1.3 Controlled Voltage Source	114
2.1.4 Controlled Current Source	115
2.1.5 Combination of Energy Sources	116
2.1.6 Voltage Sources in Series	116

2.1.7	Current Sources in Parallel	116
2.1.8	Voltage Sources in Parallel and Current Sources in Series & Parallel	117
2.1.9	Source Transformations	118
2.1.10	Source Shifting	119
2.2	Loop or Mesh Analysis and Nodal Analysis.....	122
2.3	Loop Analysis For D.C. Circuits	122
2.3.1	Redundant Elements	123
2.3.2	Identification of independant loops	123
2.3.3	Loop Analysis using Independent Voltage Sources	124
2.3.4	Loop Analysis using Independent Current Sources (Super Mesh)	127
2.3.5	Loop Analysis using Independent Voltage and Current Sources	128
2.4.	Nodal Analysis.....	131
2.4.1	Identification of Independant Nodes	132
2.5	Nodal Analysis For D.C. Circuits	133
2.5.1	Nodal Analysis using Independent Current Sources	133
2.5.2	Nodal Analysis using Independent Voltage Sources (Super Nodes).....	135
2.5.3	Nodal Analysis using Independent Voltage and Current Sources	137
2.6	Nodal Analysis with Dependent Sources	144
	Comprehension - 2	145
	Exercise - 2.....	147

CHAPTER 3

FUNDAMENTALS OF ALTERNATING CURRENT

3.1	Introduction	151
3.2	Generation of Alternating Voltages & Currents	151
3.2.1	D.C. Waveform or Steady Waveform	152
3.2.2	A.C. Waveforms	152
3.2.3	Periodic and Aperiodic Waveforms	153
3.2.4	Sinusoidal Waveforms	154
3.2.5	Generation of Sinusoidal Waveforms	156

3.3 Expression for the E.M.F. Generated by a Single Phase Alternator	158
3.3.1 Time Period (T).....	160
3.3.2 Amplitude	160
3.3.3 Cycle	160
3.3.4 Frequency	160
3.3.5 Relation between Frequency and Time Period	160
3.3.6 Relation between Frequency and Angular Velocity	161
3.3.7 Relationship Between Frequency, Speed and Number of Pole Pairs	161
3.3.8 Average Value of an Alternating Current	162
3.3.9 Root Mean Square (RMS) Value of an Alternating Current	165
3.3.10 Form Factor and Peak Factor	169
3.4 Non-Sinusoidal Waveforms	173
3.4.1 R.M.S. & Average Values of Halfwave Rectifier Output	173
3.4.2 R.M.S. & Average Values of Fullwave Rectifier Output	175
3.5 Different Forms of Representing Alternating Quantities	187
3.5.1 Phasor Representation of an Alternating Quantity	187
3.5.2 Lagging/Leading Waveforms with Phase & Phase Difference	190
3.5.3 Rectangular Coordinates Representation	191
3.5.3.1 j-Operator	191
3.5.3.2 Phasor Represented in Rectangular Coordinate Components ...	192
3.5.3.3 Trigonometrical Form of Phasor Representation	193
3.5.3.4 Exponential Form of Phasor Representation	194
3.5.3.5 Polar Form of Phasor Representation	194
3.6 Arithmetic Operations of Phasors	195
3.6.1 Addition and Subtraction of Phasors	195
3.6.2 Multiplication and Division of Phasors	196
3.6.3 Power and Roots of Vectors	197
3.6.3.1 Powers	197
3.6.3.2 Roots	197
3.6.4 Conjugate of a Phasor and Rationalization	198

3.7 Instantaneous & Average Power in A.C. Circuits	202
3.7.1 A.C. Circuit with Pure Resistance As Load	203
3.7.2 A.C. Circuit with Pure Inductance as Load	206
3.7.3 A.C. Circuit with Pure Capacitance as Load	209
Comprehension - 3	215
Exercise - 3	217

CHAPTER 4

A.C. CIRCUITS

A.C. CIRCUITS - I - SINGLE PHASE CIRCUITS

4.1 Introduction	221
4.2 Power and Power Factor in Single Phase A.C. Circuits	222
4.3 A.C. Series Circuits	222
4.3.1 R-L Series Circuit with A.C. Supply	222
4.3.2 Power Factor	225
4.3.3 Voltage Drop Triangle	226
4.3.4 Complex Power	227
4.3.5 VA or KVA Triangle	228
4.3.6 Wattfull and Wattless Component of Current	229
4.3.7 R-C Series Circuit with A.C. Supply	232
4.3.8 Power Factor	235
4.3.9 Voltage Drop Triangle	236
4.3.10 Complex Power	236
4.3.11 VA or KVA Triangle	237
4.3.12 Wattfull and Wattless Component of Current	237
4.3.13 Admittance & Admittance Triangle	239
4.3.14 R-L-C Series Circuit	241
4.3.15 A.C. Series Circuit with Two or More Impedances	243

4.4 A.C. Parallel Circuits	244
4.4.1 A.C. Parallel Circuit with Two or More Impedances	245
4.5 A.C. Series-Parallel Circuit	247
4.6 A.C. Star-Delta Connected Circuits	251
4.7. Importance of Power Factor	256
4.8 Features and Uses of A.C. Single Phase Circuits	256
4.9. Single Phase Circuits with Variable Elements-Resonance	257
4.10 Resonance in A.C. Circuits	258
4.10.1 Frequency Variation	258
4.10.2 Series Resonance	258
4.10.3 Series Resonance Frequency	260
4.10.4 Effects of Series Resonance	264
4.10.5 Selectivity & Bandwidth	266
4.10.6 Effect of Resistance in Series Resonance	271
4.10.7 Parallel Resonance	273
4.10.8 Parallel Resonant Frequency	274
4.10.9 Effects of Parallel Resonance	276
4.10.10 Quality Factor of a Parallel Resonant Circuit	277
4.10.11 Comparison of Series and Parallel Resonant Circuits	280
4.11 Single Phase Circuits with Variable Elements- Current Locus Diagrams	283
4.11.1 Series RL And RC Circuits with Variable R & Constant Reactance	284
4.11.1.1 RL Circuit with Variable Resistance	285
4.11.1.2 RC Circuit with Variable Resistance	287
4.11.2 Locus of Voltage	290
4.11.2.1 RL Circuit with Variable Resistance	290
4.11.2.2 RC Circuit with Variable Resistance	291
4.11.2.3 Series RL and RC Circuits with Variable Reactance & Constant R	291
4.11.2.4 RL Circuit with Variable Reactance	292
4.11.2.5 RC Circuit with Variable Reactance	295

4.11.2.6 Properties of Constant Reactance, Variable Resistance	298
4.11.2.7 Maximum Current	298
4.11.2.8 Maximum Power Supplied to the Circuit	298
4.11.2.9 Power Factor at Maximum Power Condition	299
4.11.3 Properties of Constant Resistance, Variable Reactance	300
4.11.3.1 Maximum Current	300
4.11.3.2 Maximum Power Supplied to the Circuit	300
4.11.3.3 Power Factor at Maximum Power Condition	300
4.11.3.4 Points to be Considered in Locus Diagrams	300
Comprehension - 4	305
Exercise - 4	309

CHAPTER 5

NETWORK THEOREMS

5.1 D.C. Network Theorems.....	315
5.1.1 Introduction to Network Theorems	315
5.1.2 Theorems in A.C. Circuits	316
5.2 Network Classification	316
5.2.1 Linear Networks	316
5.2.2 Passive Networks	316
5.2.3 Lumped Networks	317
5.2.4 Bilateral Networks	318
5.2.5 Time Invariant Networks	318
5.2.6 Reciprocity	318
5.3 Superposition Theorem for D.C. Excitation	318
5.4 Thevenin's Theorem for D.C. Excitation	323
5.5 NORTON's Theorem for D.C. Excitation	333
5.6 Maximum Power Transfer Theorem for D.C. Excitation.....	337
5.7 Superposition Theorem for A.C. Excitation	341
5.8 Thevenin's Theorem for A.C. Excitation	344

5.9	Norton's Theorem for A.C. Excitation	346
5.10	Maximum Power Transfer Theorem for A.C. Excitation	349
5.11	Reciprocity Theorem for A.C and D.C Excitations	353
5.12	Tellegen's Theorem for D.C and A.C Excitations	357
5.13	Millman's Theorem for A.C and D.C Excitations	360
5.14	Compensation Theorem for A.C. and D.C. Excitations	362
	Comprehension - 5	365
	Exercise - 5.....	367

CHAPTER 6

SEMICONDUCTOR DIODES, RECTIFIERS AND FILTERS

6.1	Introduction	373
6.1.1	Theory of p-n Junction	373
6.2	p-n junction as a Diode	375
6.2.1	Reverse Bias	375
6.2.2	Forward Bias	376
6.2.3	Ohmic Contact	376
6.2.4	Forward Current	377
6.3	Energy Band Diagram	377
6.3.1	The Current Components in a p-n Junction Diode	381
6.4	Diode Equation	382
6.5	Volt-Ampere Characteristics	385
6.5.1	Cut in Voltage V_γ	386
6.6	Temperature Dependance.....	386
6.6.1	Application of p-n Junction Diode	388
6.7	Ideal vs Practical Diode.....	388
6.8	Static and Dynamic Resistances	390
6.9	Equivalent Circuits	391

6.10 Diffusion Capacitance	392
6.10.1 Derivation for CD	393
6.11 Transition Capacitance	395
6.11.1 Alloy Junction	396

RECTIFIERS AND FILTERS

6.12 p-n Junction as a Rectifier	399
6.13 Half Wave Rectifier	399
6.14 Reading of A.C Ammeter	401
6.15 Peak Inverse Voltage	402
6.15.1 Regulation	403
6.15.2 Expression for V_{DC} the Output DC Voltage	403
6.15.3 Power Supply Specifications	405
6.16 Ripple Factor.....	405
6.17 Half Wave Rectifier Circuit (HWR)	407
6.17.1 Ratio of Rectification (η) : $\frac{P_{DC}}{P_{AC}}$	408
6.17.2 Ratio of Rectification for Half Wave Rectifier	408
6.17.3 Disadvantages of Half Wave Rectifier	409
6.18 Full Wave Rectifier (FWR)	410
6.18.1 Ripple Factor	411
6.18.2 Regulation for FWR	412
6.18.3 Ratio of Rectifications	412
6.18.4 Peak Inverse Voltage (PIV) for Full Wave Rectifier	413
6.18.5 D.C. Saturation	413
6.19 Bridge Rectifiers	413
6.19.1 Advantages of Bridge Rectifier	414
6.19.2 Disadvantages	414

6.20 The Harmonic Components in Rectifier Circuit	415
6.21 Filters	416
6.22 Inductor Filter Circuits	416
6.22.1 Ripple Factor	418
6.22.2 Regulation	418
6.22.3 Voltage Doubler Circuit	422
6.23 Capacitor Filter	423
6.23.1 Ripple Factor for C Filter	425
6.24 LC Filter	427
6.24.1 Ripple Factor in LC Filter.....	427
6.24.2 Bleeder Resistance	428
6.24.3 Swinging Choke	429
6.25 CLC or π Filter	432
6.26 π Section Filter with a Resistor Replacing the Inductor	433
6.27 Filter Circuits	434
6.27.1 Expression for Ripple Factor for π Filter	434
6.27.2 Half Wave Voltage Doubler Circuit	435
6.27.3 Full Wave Voltage Doubler	436
6.27.4 Voltage Tripler	437
6.27.5 Voltage Quadrupler	437
6.27.6 Peak to Peak Detector	437
6.27.7 Multiple LC Filters	442
6.27.8 Specification of a Power Supply	443
Summary	448
Objective Type Questions	449
Essay Type Questions	450
Multiple Choice Questions	451
Conceptual Questions (Interview Questions)	452

CHAPTER 7

BJT AND TRANSISTOR CONFIGURATIONS

7.1 Transistor Construction	455
7.1.1 Grown Type	455
7.1.2 Alloy Type	455
7.1.3 Manufacture of Grown Junction Transistor	455
7.1.4 Diffusion Type	456
7.1.5 Epitaxial Type	457
7.2 Bipolar Junction Transistor (BJT)	457
7.2.1 Principle of Operation	458
7.3 Transistor Current Components.....	459
7.4 Amplifying Action	461
7.5 Types of Transistor Configuration	462
7.6 Common Emitter Configuration (C.E)	462
7.6.1 Input Characteristics	462
7.6.2 Output Characteristics	463
7.6.2.1 Test for Saturation	464
7.6.2.2 Common Emitter Cut Off Region	464
7.7 Reverse Collector Saturation Current I_{CBO}	466
7.7.1 Saturation Resistance	466
7.7.2 DC Current Gain b_{dc}	466
7.7.3 Test for Saturation	467
7.8 Common Base Configuration (C.B)	467
7.8.1 Early Effect	469
7.9 The Common Collector Configuration (C.C)	469
7.9.1 Parameters	471
7.10 Analytical Expressions for Transistor Characteristics	472
7.11 Ebers - Moll Model of a Transistor	473

7.12 Transistor in Cut-Off Region under C.E. Configuration	473
7.12.1 Short Circuit Base	474
7.13 Transistor Biasing	482
7.13.1 Operating Point	482
7.13.2 Static Load Line or DC Load Line	484
7.14 Biasing Circuits	485
7.15 Need for Biasing/Importance of Biasing	485
7.16 Fixed Bias Circuit or (Base Bias Circuit)	485
7.17 Bias Stability	486
7.18 Thermal Instability	487
7.19 Stability Factor ‘S’	487
7.20 Self Bias or Emitter Bias Circuit	489
7.21 Stabilization Against Variation in i_{c0} and v_{be} and β	490
7.22 Stability Factor S'	491
7.23 Stability Factor S''	494
7.24 Practical Considerations.....	495
7.25 Bias Compensation	495
7.26 Collector to Base Bias	498
7.27 Diode Compensation for V_{BE}	501
7.28 Diode Compensation for I_{CO}	502
7.29 Biasing Circuits for Linear Integrated Circuits	503
7.30 BJT Modeling using h-parameters	504
7.31 Simplified Transistor Hybrid Model	504
7.32 Determination of h-Parameters from Transistor Characteristics	506
7.33 Measurement of h-Parameters	508
7.34 Analysis of CE, CB and CC Configurations using h-parameters	509
7.34.1 Input Impedance (Z_i)	511
7.34.2 Voltage Gain (A_V)	512

7.34.3 Output Admittance (Y_o)	512
7.34.4 Voltage Gain (A_{vs}) considering Source Resistance R_s	513
7.34.5 Current Gain (A_{IS}) Considering Source Resistance.....	513
7.34.6 Power Gain (A_p).....	514
7.35 Comparison of CE, CB, CC Configurations using h-parameters	515
Summary	518
Objective Type Questions	519
Essay Type Questions	520
Multiple Choice Questions	521
Conceptual Questions (Interview Questions)	523

CHAPTER 8

JFET AND SPECIAL PURPOSE DEVICES

8.1 Junction Field Effect Transistor (JFET).....	525
8.1.1 JFET	526
8.2 Construction	526
8.3 Principle Operation	527
8.4 Symbol	531
8.4.1 n-channel JFET	531
8.4.2 p-channel JFET	531
8.5 Pinch off Region.....	532
8.6 JFET Volt-Ampere Characteristics	534
8.6.1 Expression for V_{GS}	535
8.6.2 The ON Resistance $r_{ds} (\text{ON})$	536
8.7 Transfer Characteristics of FET	536
8.8 Comparison between BJT and FET	537
8.9 Small Signal Model	537
8.10 FET Biasing for Zero Drift Current	538

SPECIAL PURPOSE DEVICES

8.11 Break Down Mechanisms in Semiconductor Diodes	542
8.11.1 Avalanche Breakdown	542
8.11.2 Zener Breakdown	542
8.11.3 Thermal Breakdown	542
8.12 Use of Zener Diode as Regulator	543
8.12.1 Zener Voltage Regulator Circuit	544
8.12.2 Shunt Regulator	545
8.13 The Tunnel Diode.....	548
8.13.1 Principle of Operation	548
8.13.2 Characteristics of a Tunnel Diode	549
8.14 Varactor Diode	551
8.15 Silicon Controlled Rectifier	553
8.15.1 Annular Type of Construction of SCR	553
8.15.2 Static Characteristics	554
8.15.3 Analysis of the Operation of SCR	555
8.15.4 Anode to Cathode Voltage - Current Characteristics	558
8.16 DIAC	559
8.16.1 Diagram for Basic Construction and Symbol	559
8.16.2 Characteristics of DIAC	559
8.17 TRIAC	560
8.17.1 Construction	561
8.17.2 Characteristics	561
Summary	562
Objective Type Questions	563
Essay Type Questions	563
Multiple Choice Questions.....	563
Conceptual Questions (Interview Questions)	565