

## **Contents**

---

Preface .....	(vii)
---------------	-------

### **CHAPTER 1**

#### **Measuring Instruments**

1.1	Introduction.....	1
1.2	Classification of Measuring Instruments .....	1
1.2.1	Absolute Instruments.....	1
1.2.2	Secondary Instruments .....	2
1.3	Essentials of Indicating Instruments.....	2
1.4	Deflecting System .....	3
1.5	Controlling System.....	4
1.5.1	Spring Control.....	4
1.5.2	Gravity Control .....	5
1.5.3	Comparison of Controlling Systems .....	6
1.6	Damping Torque.....	7
1.6.1	Air Friction Damping .....	8
1.6.2	Fluid Friction Damping .....	8
1.6.3	Eddy Current Damping .....	9
1.7	Permanent Magnet Moving Coil (PMMC).....	9
1.7.1	Advantages.....	10
1.7.2	Disadvantages .....	10
1.7.3	Torque Equation .....	11
1.8	D' Arsonval Galvanometer.....	12
1.8.1	Torque Equation .....	14
1.9	Intrinsic Constants of Galvanometer .....	15
1.9.1	Constant of Inertia ( $J$ ) .....	15
1.9.2	Control Constant.....	16
1.9.3	Displacement Constant ( $G$ ) .....	16
1.9.4	Damping Constant.....	16

**(x)      Contents**

---

1.10	Dynamic behaviour of Galvanometer .....	16
1.11	Undamped Motion .....	18
1.12	Underdamped Motion .....	19
1.13	Critically Damped Motion.....	22
1.14	Overdamped Motion.....	23
1.15	Logarithmic Decrement .....	24
1.16	Settling Time.....	27
1.17	Effect of External Resistance on Damping .....	28
1.17.1	Mechanical Damping .....	28
1.17.2	Electromagnetic Damping .....	28
1.18	Critical Resistance for Damping .....	30
1.19	Sensitivity of Galvanometer .....	30
1.19.1	Voltage Sensitivity .....	31
1.19.2	Current Sensitivity.....	31
1.19.3	Megohm Sensitivity.....	31
1.20	Errors in Moving Coil Instruments .....	32
1.20.1	Temperature Error .....	32
1.20.2	Mechanical Unbalance .....	32
1.20.3	Frictional Error .....	33
1.20.4	Observational Error .....	33
1.20.5	Ageing .....	33
1.21	Moving Iron Instrument .....	33
1.21.1	Attraction (or single-iron) Type M.I Instrument .....	34
1.21.2	Torque Equation of Moving Iron Instruments .....	35
1.22	Moving Iron Repulsion Type Instrument (Double-Iron) Type .....	37
1.22.1	Radial Vane Repulsion Type Instrument .....	37
1.22.2	Concentric Vane Repulsion Type Instrument .....	38
1.23	The advantages and disadvantages of M.I. Instrument .....	39
1.23.1	Advantages .....	39
1.23.2	The main disadvantages are.....	39
1.24	Errors in M.I Instrument.....	40
1.24.1	Hysteresis Error .....	40
1.24.2	Stray Magnetic Fields .....	40
1.24.3	Temperature Error.....	40
1.25	Errors with A.C only .....	41
1.25.1	Frequency Error .....	41

1.25.2	Reactance of Instrument Coil .....	41
1.25.3	Eddy Current Error .....	42
1.25.4	Hysteresis Error .....	42
1.26	Comparison between moving Coil and moving Iron Instrument .....	42
1.27	Basic D.C Ammeter .....	43
1.28	Multi Range Ammeters.....	44
1.29	The Aryton Shunt or Universal Shunt.....	45
1.30	Requirement of a Shunt .....	46
1.31	Precautions to be taken while using an Ammeter .....	46
1.32	Basic D.C Voltmeter .....	46
1.32.1	Multirange Voltmeter.....	48
1.32.2	Practical Multirange Voltmeter.....	48
1.33	Sensitivity of Voltmeters.....	49
1.34	Loading Effect .....	51
1.35	Requirements of a Multiplier .....	51
1.36	Precautions to be taken while using a Voltmeter.....	51
1.37	Ammeter and Voltmeter.....	51
1.38	Type of Electrostatic Voltmeters.....	55
1.38.1	Quadrant – Type Electrostatic Voltmeter.....	55
1.38.2	Heterostatic Connection.....	56
1.38.3	Theory of Heterostatic Connection .....	57
1.38.4	Idiostatic Connection.....	60
1.38.5	Theory of Idiostatic Connection .....	61
1.39	Kelvin Multicellular Voltmeter.....	61
1.40	Attracted Disc Electrostatic Voltmeter .....	62
1.41	Theory of Attracted Disc Type Voltmeter.....	63
1.42	Kelvin Absolute Electrometer.....	64
1.43	Advantages and Disadvantages of Electrostatic Instruments.....	66
1.44	Extension of Range of Electrostatic Voltmeter .....	66
<b>Problems with Solutions .....</b>		<b>70</b>
<b>Review Questions .....</b>		<b>85</b>
<b>Quiz Questions .....</b>		<b>86</b>
<b>Questions and Answers .....</b>		<b>91</b>

## **CHAPTER 2**

### **Instrument Transformers**

2.1	Introduction.....	99
2.2	Current Transformer .....	99
2.2.1	Constructional Details of Current Transformer .....	100
2.2.2	Working Principle.....	101
2.2.3	Construction of Current Transformers.....	101
2.2.4	Wound Type.....	102
2.2.5	Bar Type Current Transformer .....	103
2.2.6	Theory of Current Transformers .....	103
2.2.7	Derivation of Actual Ratio.....	105
2.3	Derivation of Phase Angle ( $\theta$ ) of Transformer .....	107
2.4	Errors in Current Transformer.....	107
2.4.1	Ratio Error.....	107
2.4.2	Phase Angle Error.....	108
2.5	Causes of Errors in Current Transformer.....	109
2.6	Characteristic of Current Transformer .....	109
2.7	Why Current Transformer of Secondary should not be open? .....	110
2.8	Potential Transformer (PT).....	110
2.8.1	Constructional Details.....	111
2.8.2	Theory of Potential Transformer .....	111
2.8.3	Derivation of Actual Ratio.....	113
2.8.4	Derivation of Phase Angle ' $\theta'$ .....	115
2.9	Characteristic of Potential Transformers.....	116
2.10	Errors in Potential Potential Transformer .....	117
2.11	Application of Current Transformer and Potential Transformer .....	117
2.12	Advantages and Disadvantages of Instrument Transformer .....	117
2.13	Difference between Instrument and Power Transformers .....	117
2.14	Power Factor Meter (p.f meter).....	118
2.14.1	Electrodynamometer Type Power Factor Meter .....	119
2.15	Moving Iron Power Factor Meter .....	120
2.15.1	Rotating Field Type Moving Iron Power Factor Meter .....	121
2.15.2	Alternating Field Type Moving Iron Power Factor Meter .....	122

---

2.16	Frequency Meters .....	123
2.16.1	Vibrating Reed Type Frequency Meter .....	124
2.16.2	Electrical Resonance Type Frequency Meter .....	125
2.16.3	Weston Frequency Meter.....	127
2.17	Synchrosopes .....	128
2.17.1	Weston Synchronoscope (or) Electrodynamometer Type Synchroscope .....	128
2.17.2	Moving Iron Synchrosopes.....	129
	<b>Problems with Solutions .....</b>	<b>130</b>
	<b>Review Questions .....</b>	<b>134</b>
	<b>Quiz Questions.....</b>	<b>136</b>
	<b>Questions and Answers .....</b>	<b>139</b>

## CHAPTER 3

### Measurement of Power

3.1	Introduction.....	142
3.2	Electrodynamometer Type Instruments.....	144
3.2.1	Advantages and Disadvantages of Electrodynamic Instruments .....	147
3.2.2	Errors in Electrodynamometer Instruments .....	148
3.2.3	Comparison of various Types of Instruments .....	148
3.3	Single Phase Dynamometer Wattmeter.....	149
3.3.1	Reading on Wattmeter .....	151
3.3.2	Shape of Scale of Electrodynamometer Wattmeter (Theory) .....	152
3.4	Error due to Pressure Coil Inductance.....	153
3.5	Compensation for Inductance of Pressure Coil.....	155
3.6	Error due to Pressure Coil Capacitance.....	156
3.7	Error due to Mutual Inductance Effect.....	156
3.8	Error caused because of Connections .....	157
3.9	Compensation .....	158
3.10	Low Power Factor Electrodynamic Type Wattmeter .....	159
3.11	Power in Three Phase System .....	161
3.12	The Main Difference between LPF and UPF Wattmeters .....	162

---

**(xiv)    Contents**

3.13	Examples of Wattmeter Connections and Corresponding Readings .....	162
3.13.1	Simple (or) One Wattmeter Method .....	165
3.13.2	Disadvantages .....	167
3.14	3-Wattmeter Method .....	167
3.15	Blondel's Theorem.....	168
3.16	Two Wattmeter Method .....	168
3.16.1	Proof of 2-Wattmeter Method .....	169
3.16.2	Power Factor Calculation by Two-wattmeter Method.....	172
3.17	Effect of Power Factor on Wattmeter Readings .....	173
3.18	Reactive Volt-Amperes by Two Wattmeter Method .....	173
3.19	Disadvantages and Advantages of Two Wattmeter Method .....	174
3.20	Modified Version of 2-Wattmeter as One Wattmeter Method.....	174
3.21	One wattmeter Method for Reactive Volt Amperes Measurement....	176
3.22	Extension of Range of Wattmeter using Instrument Transformer .....	176
3.22.1	Phasor Diagrams and Correction Factors.....	177
3.22.2	Correction Factor .....	179
3.23	3- $\phi$ Power Measurement using Current Transformer and Power Potential Transformer .....	179
3.24	The Advantages and Disadvantages of Instrument Transformer for Extension of Range of A.C. Instrument .....	180
3.25	3- $\phi$ Wattmeter .....	180
3.25.1	Elimination of Mutual Effects between the Two Elements of the Wattmeter .....	182
<b>Problems with Solutions .....</b>		<b>182</b>
<b>Review Questions .....</b>		<b>187</b>
<b>Quiz Questions .....</b>		<b>188</b>
<b>Questions and Answers .....</b>		<b>189</b>

**CHAPTER 4****Measurement of Energy**

4.1	Introduction.....	193
4.2	Single Phase Energy Meter (1- $\phi$ ).....	194

---

4.3	Construction of Induction Type Energy Meters.....	195
4.3.1	Driving System.....	195
4.3.2	Moving System.....	195
4.3.3	Braking System.....	196
4.3.4	Registering (Counting) Mechanism System.....	196
4.4	Theory and Operation of Single Phase Energy Meters .....	197
4.5	Torque Equation .....	199
4.6	Errors and Compensations.....	201
4.6.1	Temperature Effect and Compensation.....	201
4.6.2	Lag Adjustment or Power Factor Adjustment.....	201
4.6.3	Light Load Adjustment or Friction Compensation.....	203
4.6.4	Creeping or Creeping Compensation.....	204
4.6.5	Main Speed Adjustment .....	204
4.6.6	Over-load Compensation .....	204
4.6.7	Voltage Compensation.....	205
4.7	Advantages and Disadvantages of Induction Type Energy Meter .....	205
4.8	Three Phase Energy Meter.....	206
4.9	Three Element Energy Meter .....	206
4.9.1	Two Element Energy Meter.....	208
4.10	Calibration of an Energy Meter .....	209
4.11	Current Transformer and Potential Transformer uses in Energy Measurement .....	210
4.12	Average Demand Indicator (or) (Merz Price Maximum Demand Indicator).....	212
4.12.1	Construction and Operation .....	212
4.12.2	Advantages.....	213
4.12.3	Disadvantages .....	213
4.13	Phantom Loading .....	214
4.14	Testing of Energy Meters.....	214
4.14.1	Testing of Meter using Rotating Sub Standard Meter .....	215
4.14.2	Meter Testing Circuit using Phase Shifting Device .....	215
4.15	Trivector Meter .....	217
4.16	Tariff .....	219
4.17	Objectives of Tariff.....	219
4.18	Important Terms and Factors.....	219

**(xvi)    Contents**

---

4.19	Types of Tariff .....	220
4.19.1	Simple Tariff .....	220
4.19.2	Flat Rate Tariff.....	220
4.19.3	Block Rate Tariff.....	221
4.19.4	Two-Part Tariff.....	221
4.19.5	Three Part Tariff.....	222
4.19.6	Power-Factor Tariff.....	222
	<b>Review Questions .....</b>	<b>223</b>
	<b>Quiz Questions .....</b>	<b>224</b>
	<b>Questions and Answers .....</b>	<b>225</b>

## **CHAPTER 5**

### **Potentiometers**

5.1	Introduction.....	229
5.2	Principle of Potentiometer.....	230
5.3	Potentiometers for use with Direct Current (or) Slide Wire D.C. Potentiometer.....	231
5.3.1	Precautions .....	232
5.3.2	Standardization of Potentiometer .....	233
5.4	The Crompton's D.C. Potentiometer.....	233
5.5	Duo-range Potentiometer .....	235
5.5.1	Advantages of Duo-range Potentiometer.....	238
5.5.2	Simple Potentiometer with Independent Calibrating Circuit .....	238
5.6	Vernier Potentiometer.....	239
5.7	Brook's Deflectional Potentiometer.....	241
5.8	Potentiometer with True Zero .....	242
5.9	Volt-Ratio Box .....	242
5.10	Applications of D.C Potentiometer .....	243
5.10.1	Calibration of Voltmeter .....	243
5.10.2	Calibration of Ammeter .....	244
5.10.3	Measurement of Power .....	245
5.10.4	Calibration of Wattmeter .....	246
5.10.5	Measurement of Resistance .....	247

5.11	A.C Potentiometer .....	248
5.11.1	The Basic Requirement of A.C Potentiometers .....	249
5.12	Drysdale-Tinsley Polar Type A.C Potentiometer.....	250
5.13	Standardisation of Drysdale-Tinsley A.C Potentiometer.....	251
5.13.1	Measurement of Unknown e.m.f.....	251
5.13.2	Transfer Instrument.....	252
5.14	Self Balancing Potentiometer .....	253
5.15	Gall-Tinsley Co-ordinate Type A.C Potentiometer .....	254
5.15.1	Measurement of Unknown e.m.f.....	256
5.15.2	Measurement of Unknown Inductance using A.C Potentiometers.....	256
5.15.3	Measurement of Unknown Capacitance Using A.C Potentiometer .....	258
5.16	The Application of Potentiometers .....	259
5.17	Errors in a Potentiometers .....	260
5.18	Apply a Correction for Thermo-emf in D.C Potentiometer Measurement .....	260
5.19	Comaparison between A.C. and D.C. Potentiometers .....	261
5.20	The Modifications are needed in a D.C. Potentiometers to be used for A.C Application are .....	261
5.21	Applications of A.C Potentiometers .....	262
	<b>Problems with Solutions .....</b>	<b>263</b>
	<b>Review Questions .....</b>	<b>272</b>
	<b>Quiz Questions .....</b>	<b>273</b>
	<b>Questions and Answers .....</b>	<b>274</b>

## **CHAPTER 6**

### **Resistance Measurements**

6.1	Introduction.....	277
6.2	Classification of Low Resistance.....	278
6.2.1	Voltmeter-Ammeter Method.....	278
6.2.2	Kelvin Bridge - Measurement of Low Resistance.....	281

---

**(xviii) Contents**

6.2.3	Kelvin's Double Bridge Method for Low Resistance Measurement.....	284
6.2.4	Practical Kelvin's Double Bridge.....	287
6.2.5	Potentiometer Method .....	288
6.3	Medium Resistance.....	288
6.3.1	Ammeter-Voltmeter Method .....	289
6.3.2	Substitution Method.....	290
6.3.3	Wheatstone Bridge Method.....	291
6.3.4	Industrial Form of Wheatstone Bridge .....	292
6.3.5	Sensitivity of Wheatstone Bridge .....	293
6.4	Wheatstone Bridge under Small Unbalance .....	294
6.4.1	Thevenin's Equivalent and Galvanometer Current.....	296
6.4.2	Galvanometer Current under Unbalanced Condition .....	297
6.4.3	Sensitivity of Bridge in terms of Current Sensitivity of Galvanometer .....	297
6.5	Measurement Errors or the Precision Measurement of Wheatstone Bridge .....	298
6.6	Advantages of Wheatstone Bridge.....	299
6.7	Limitations of Wheatstone Bridge.....	299
6.8	Application of Wheatstone Bridge .....	299
6.9	Carey-Foster Slide Wire Bridge .....	300
6.10	Methods for Measurement of High Resistances.....	302
6.11	Direct Deflection Method .....	302
6.12	Loss of Charge Method.....	304
6.13	Errors in Loss of Charge Method .....	307
6.13.1	Error due to Leakage and Absorption .....	307
6.13.2	Error due to Variation in Insulation Resistance due to Variation in Temperature .....	308
6.13.3	Error due to Time of Application of Voltage .....	308
6.14	Megohm Bridge.....	308
6.15	Megger.....	309
6.15.1	Construction .....	310
6.15.2	Working.....	311
6.15.3	Applications.....	311
6.16	Bridge in Controlled Circuits .....	311

6.17	Difficulties in the Measurement of High Resistance .....	312
6.18	Use of Guard Circuits.....	313
<b>Problems with Solutions .....</b>		<b>315</b>
<b>Review Questions .....</b>		<b>327</b>
<b>Quiz Questions .....</b>		<b>328</b>
<b>Questions and Answers .....</b>		<b>329</b>

## CHAPTER 7

### A.C Bridges

7.1	Introduction.....	331
7.2	Advantages of Bridge Circuit and Applications .....	331
7.3	Types of Bridges.....	332
7.4	AC Bridge .....	332
7.4.1	Bridge Balance Equation .....	333
7.4.2	Sources and Detectors .....	335
7.5	Inductance Comparison Bridge.....	336
7.6	Maxwell's Bridge .....	337
7.7	Maxwell's Inductance Bridge.....	337
7.8	Maxwell's Inductance Capacitance Bridge .....	338
7.9	Advantages of Maxwell Bridge .....	340
7.10	Disadvantages of Maxwell Bridge .....	340
7.11	The Different Sources of Errors in A.C Bridges.....	341
7.11.1	Eddy Current Errors.....	341
7.11.2	Stray Conductance Effects .....	341
7.11.3	Errors due to Electromagnetic Coupling.....	341
7.11.4	Errors due to Electrostatic Coupling.....	341
7.11.5	Frequency Errors.....	342
7.11.6	Residual Errors.....	342
7.12	Anderson Bridge.....	342
7.12.1	Advantages of Anderson Bridge .....	345
7.12.2	Disadvantages of Anderson Bridge .....	345
7.13	Hay's Bridge .....	346
7.13.1	Advantage of Hay's Bridge .....	349
7.13.2	Disadvantage of Hay's Bridge .....	349
7.14	Capacitance Comparison Bridge .....	349

---

**(xx)    Contents**

---

7.15	Schering Bridge .....	350
7.16	Power Factor and Loss Angle .....	352
7.16.1	Power Factor (P.F) .....	352
7.16.2	Loss Angle ( $\delta$ ).....	353
7.16.3	Dissipation Factor (D) .....	354
7.17	High Voltage Schering Bridge .....	355
7.18	Wien Bridge .....	356
7.18.1	Applications.....	358
7.19	De Sauty Bridge .....	359
7.19.1	Modified De Sauty Bridge .....	360
7.20	Owen's Bridge.....	362
7.20.1	Advantages of Owen's Bridge .....	364
7.20.2	Disadvantages of Owen's Bridge .....	364
7.20.3	Application of Owen's Bridge.....	364
7.21	Heaviside Mutual Inductance Bridge.....	366
7.22	Campbell's Modification of Heaviside Bridge .....	368
7.23	Heaviside Campbell Equal Ratio Bridge .....	370
7.24	Shielding and Grounding of Bridges .....	371
	<b>Problems with Solutions .....</b>	<b>375</b>
	<b>Review Questions .....</b>	<b>393</b>
	<b>Quiz Questions.....</b>	<b>394</b>
	<b>Questions and Answers .....</b>	<b>395</b>

**CHAPTER 8****Magnetic Measurements**

8.1	Introduction.....	400
8.1.1	D.C Tests of Ballistic Tests.....	400
8.1.2	A.C Testing .....	401
8.1.3	Steady State Tests.....	401
8.2	Ballistic Galvanometer .....	401
8.2.1	The Construction of a Moving Coil Ballistic Galvanometer.....	402
8.2.2	Theory of Ballistic Galvanometer .....	403
8.2.3	Logarithmic Decrement .....	406
8.3	Flux Meter.....	408

8.4	Comparision between Flux Meter and Ballistic Galvanometer .....	410
8.5	Measurement of Flux Density (B).....	411
8.5.1	Theory of the Flux Density Measurement.....	411
8.5.2	Correction of Air Flux .....	413
8.6	Measurement of Magnetising Force H .....	413
8.7	Magnetic Potentiometer.....	414
8.8	Measurement of Leakage Factor with Flux Meter .....	416
8.9	Determination of B-H Curve.....	417
8.9.1	Method of Reversals.....	418
8.9.2	Sources of Errors and Method of Reducing .....	419
8.9.3	Step by Step Method .....	420
8.9.4	Advantages of Method of Reversals Over Step-by-Step Method .....	421
8.10	Magnetic Testing under A.C Conditions.....	421
8.10.1	Hysteresis Loss.....	422
8.10.2	Eddy Current Loss.....	423
8.11	Separation of Iron Losses.....	423
8.11.1	Variation of Frequency.....	423
8.11.2	Variation of Form Factor.....	424
8.12	Methods of Measuring Iron Losses .....	425
8.12.1	Wattmeter Method .....	425
8.12.2	Bridge Methods .....	429
8.12.3	A.C Potentiometer Method .....	433
8.12.4	Oscillographic Method.....	435
8.13	Ewing Double Bar Permeameter .....	437
8.13.1	Advantage.....	438
8.13.2	Disadvantages .....	438
8.14	Illiovici Permeamter .....	438
8.15	Burrow's Permeameter .....	440
8.15.1	The Advantages of Burrow's Permeameter with Respect to Others.....	442
	<b>Problems with Solutions .....</b>	<b>442</b>
	<b>Review Questions .....</b>	<b>454</b>
	<b>Quiz Questions .....</b>	<b>455</b>
	<b>Questions and Answers .....</b>	<b>456</b>

## **CHAPTER 9**

### **Electronic Instruments**

9.1	Introduction.....	457
9.1.1	True R.M.S Voltmeter.....	458
9.1.2	Electronic Multimeter.....	459
9.1.3	Voltage Measurement .....	460
9.1.4	Resistance Measurement .....	461
9.2	Digital Voltmeters (DVM) .....	463
9.2.1	Introduction.....	463
9.2.2	Characteristic Features of DVMs .....	463
9.2.3	Application of DVMs .....	464
9.2.4	Classification of Digital Voltmeters (DVMs) .....	464
9.2.5	Advantages of DVMs .....	464
9.2.6	Q-meter .....	464
	<b>Review Questions .....</b>	<b>466</b>
	<b>Quiz Questions .....</b>	<b>467</b>
	<b>Questions and Answers .....</b>	<b>467</b>

## **CHAPTER 10**

### **Dual Trace Oscilloscope**

10.1	Voltage Measurement .....	470
10.1.1	Lissajous Figures/Patterns .....	472
10.1.2	Uses.....	473
10.1.3	Phase-angle Measurement.....	475
10.1.4	Frequency Measurement .....	476
10.1.5	Measurement Procedure.....	476
10.1.6	Digital Storage Oscilloscope.....	477
10.1.7	Applications.....	479
	<b>Review Questions .....</b>	<b>480</b>
	<b>Quiz Questions .....</b>	<b>480</b>
	<b>Questions and Answers .....</b>	<b>482</b>

**CHAPTER 11****Transducers**

11.1	Introduction.....	484
11.2	Classification of Transducers .....	485
11.3	Selection of Transducers .....	487
11.4	Strain Gauges .....	488
11.5	Theory of Strain Gauges .....	488
11.6	Linear-Variable-Differential Transformer (LVDT) .....	491
11.7	Applications .....	493
11.8	Temperature Transducers .....	493
11.9	Photoconductive Cells .....	494
11.10	Photovoltaic Cell.....	495
	<b>Review Questions .....</b>	<b>496</b>
	<b>Quiz Questions.....</b>	<b>498</b>
	<b>Questions and Answers .....</b>	<b>503</b>

**CHAPTER 12****Display Devices and Signal Generators**

12.1	Introduction.....	506
12.2	X-Y Recorders.....	509
12.3	Applications .....	510
12.4	Digital X-Y Recorders Advantages .....	511
12.5	Liquid Crystal Displays (LCDs) .....	513
12.6	Features of LCDs.....	513
12.7	Light Emitting Diode (LED) .....	514
12.8	Applications .....	517
12.9	Signal Generators.....	517
12.10	Characteristics of Signal Generators .....	517
12.11	Applications .....	517
12.12	Classification of Signal Generators .....	518
12.13	Conventional Standard Signal Generator .....	518
12.14	Modern Signal Generator .....	519

---

**(xxiv) Contents**

---

12.15	Function Generator.....	521
12.16	Application .....	522
<b>Review Questions .....</b>		<b>523</b>
<b>Quiz Questions .....</b>		<b>523</b>
<b>Questions and Answers .....</b>		<b>526</b>

**CHAPTER 13****Cathode Ray Oscilloscope**

13.1	Introduction.....	529
13.2	Analog and Digital Oscilloscopes .....	529
13.3	Cathode Ray Tube (CRT).....	531
13.3.1	Idea of Operation of CRT.....	531
13.3.2	The Deflection System.....	532
13.3.3	Displaying a Voltage Waveform .....	533
13.3.4	Pulse Generator and Sweep Generator.....	535
13.4	Digital Storage Oscilloscopes (DSO) .....	536
13.4.1	Measurement Techniques.....	537
13.4.2	Phase Difference .....	538
13.4.3	Controls .....	539
13.5	Applications of CRO .....	540
13.6	CRO Probes.....	540
13.6.1	Probe Frequency Compensation.....	542
<b>Review Questions .....</b>		<b>544</b>
<b>Quiz Questions .....</b>		<b>544</b>
<b>Questions and Answers .....</b>		<b>545</b>