

# Contents

---

<i>Preface</i> .....	(xv)
----------------------	------

## CHAPTER 1: INTRODUCTION

1.1 The Electrical Power System .....	1
1.2 Network Models .....	3
1.3 Faults and Analysis .....	3
1.4 The Primitive Network .....	4
1.5 Power System Stability .....	5
1.6 Deregulation .....	5
1.7 Renewable Energy Resources .....	6

## CHAPTER 2: GRAPH THEORY

2.1 Introduction .....	7
2.2 Definitions .....	7
2.3 Tree and Cotree .....	9
2.4 Basic Loops .....	9
2.5 Cut-Set .....	10
2.6 Basic Cut-Sets .....	10
<i>Worked Examples</i> .....	12
<i>Problems</i> .....	16
<i>Questions</i> .....	17

## CHAPTER 3: INCIDENCE MATRICES

3.1 Element Node Incidence Matrix .....	19
3.2 Bus Incidence Matrix .....	20
3.3 Branch-Path Incidence Matrix $K$ .....	21
3.4 Basic Cut-Set Incidence Matrix .....	22
3.5 Augmented Cut-Set Incidence Matrix $\tilde{B}$ .....	23
3.6 Basic Loop Incidence Matrix .....	24
3.7 Augmented Loop Incidence Matrix .....	25
3.8 Network Performance Equations .....	26
<i>Worked Examples</i> .....	29
<i>Problems</i> .....	33
<i>Questions</i> .....	33

**CHAPTER 4: NETWORK MATRICES**

4.1 Introduction .....	35
4.2 Network Matrices .....	35
4.2.1 Network Matrices by Singular Transformations .....	35
4.2.2 Network Matrices by Non-Singular Transformation .....	40
4.3 Bus Admittance Matrix by Direct Inspection .....	46
<i>Worked Examples</i> .....	50
<i>Problems</i> .....	69
<i>Questions</i> .....	70

**CHAPTER 5: BUILDING OF NETWORK MATRICES**

5.1 Introduction .....	71
5.2 Partial Network .....	71
5.3 Addition of a Branch .....	73
5.3.1 Calculation of Mutual Impedances .....	74
5.3.2 Calculation of Self Impedance of Added Branch $Z_{ab}$ .....	76
5.3.3 Special Cases .....	77
5.4 Addition of a Link .....	78
5.4.1 Calculation of Mutual Impedances .....	79
5.4.2 Computation of Self-impedance .....	80
5.4.3 Removal of Elements or Changes in Element .....	83
5.5 Removal or Change in Impedance of Elements with Mutual Impedance .....	84
<i>Worked Examples</i> .....	88
<i>Problems</i> .....	113
<i>Questions</i> .....	114

**CHAPTER 6: SYMMETRICAL COMPONENTS**

6.1 The Operator “a” .....	116
6.2 Symmetrical Components of Unsymmetrical Phases .....	117
6.3 Power in Sequence Components .....	119
6.4 Unitary Transformation for Power Invariance .....	120

**CHAPTER 7: THREE-PHASE NETWORKS**

7.1 Three-Phase Network Element Representation .....	123
7.1.1 Stationary Network Element .....	125
7.1.2 Rotating Network Element .....	125
7.1.3 Performance Relations for Primitive Three-Phase Network Element .....	126
7.2 Three Phase Balanced Network Elements .....	126
7.2.1 Balanced Excitation .....	126
7.2.2 Transformation Matrices .....	128

7.3 Three-Phase Impedance Networks.....	129
7.3.1 Incidence and Network Matrices for Three-Phase Networks.....	129
7.3.2 Algorithm for Three-Phase Bus Impedance Matrix .....	130
<i>Summary of the Formulae</i> .....	136
<i>Worked Examples</i> .....	138
<i>Problems</i> .....	150
<i>Questions</i> .....	150

**CHAPTER 8: SYNCHRONOUS MACHINE**

8.1 The Two-Axis Model of Synchronous Machine.....	153
8.2 Derivation of Park’s Two Axis Model.....	155
8.3 Synchronous Machine Analysis .....	157
8.3.1 Voltage Relations—Stator or Armature .....	158
8.3.2 Flux Linkage Relations .....	159
8.3.3 Inductance Relations .....	159
8.3.4 Flux Linkage Equations.....	162
8.4 The Transformations .....	162
8.5 Stator Voltage Equations.....	164
8.6 Steady-State Equation .....	165
8.7 Steady-State Vector Diagram.....	166
8.8 Reactances.....	167
8.9 Equivalent Circuits and Phasor Diagrams.....	170
8.9.1 Model for Transient Stability .....	170
8.10 Transient State Phasor Diagram.....	172
8.11 Power Relations .....	174
8.12 Synchronous Machine Connected through an External Reactance.....	176
<i>Worked Examples</i> .....	178
<i>Problems</i> .....	180
<i>Questions</i> .....	180

**CHAPTER 9: LINES AND LOADS**

9.1 Lines.....	181
9.1.1 Short Lines .....	181
9.1.2 Medium Lines.....	181
9.1.3 Long Lines.....	181
9.2 Transformers .....	184
9.2.1 Transformer with Nominal Turns Ratio.....	184
9.2.2 Phase Shifting Transformers .....	186
9.3 Load Modeling .....	188
9.3.1 Constant Current Model .....	191

**(x) Contents**

---

9.3.2	Constant Impedance Model .....	192
9.3.3	Constant Power Model .....	193
9.4	Composite Load .....	193
9.4.1	Dynamic Characteristics .....	194
9.5	Induction Machine Modeling .....	194
9.6	Model with Mechanical Transients .....	195
9.6.1	Power Torque and Slip .....	197
9.6.2	Reactive Power and Slip .....	198
9.6.3	Synchronous Motor .....	204
9.7	Rectifiers and Inverter Loads .....	205
9.7.1	Static Load Modeling for Load Flow Studies .....	205
9.7.2	Voltage Dependence of Equivalent Loads .....	205
9.7.3	Derivation for Equivalent Load Powers .....	206
	<i>Worked Examples</i> .....	209
	<i>Problems</i> .....	210
	<i>Questions</i> .....	210

**CHAPTER 10: POWER FLOW STUDIES**

10.1	Necessity for Power Flow Studies .....	211
10.2	Conditions for Successful Operation of a Power System .....	212
10.3	The Power Flow Equations .....	212
10.4	Classification of Buses .....	214
10.5	Bus Admittance Formation .....	215
10.6	System Model for Load Flow Studies .....	217
10.7	Gauss-Seidel Method .....	219
10.8	Gauss-Seidel Iterative Method .....	220
10.8.1	Acceleration Factor .....	221
10.8.2	Treatment of a PV Bus .....	222
10.9	Newton-Raphson Method .....	224
10.9.1	Rectangular Coordinates Method .....	225
10.9.2	The Polar Coordinates Method .....	227
10.10	Sparsity of Network Admittance Matrices .....	231
10.11	Triangular Decomposition .....	231
10.12	Optimal Ordering .....	233
10.13	Decoupled Methods .....	235
10.14	Fast Decoupled Methods .....	236

10.15	Load Flow Solution using Z Bus.....	237
10.15.1	Bus Impedance Formation .....	237
10.15.2	Addition of a Line to the Reference Bus .....	238
10.15.3	Addition of a Radial Line and New Bus .....	238
10.15.4	Addition of a Loop Closing Two Existing Buses in the System .....	239
10.15.5	Gauss – Seidel Method using Z-bus for Load Flow Solution.....	240
10.16	Convergence Characteristics .....	240
10.17	Comparison of Various Methods for Power Flow Solution.....	241
	<i>Worked Examples</i> .....	243
	<i>Problems</i> .....	276
	<i>Questions</i> .....	286

**CHAPTER 11: SHORT CIRCUIT ANALYSIS**

11.1	Per Unit Quantities .....	289
11.2	Advantages of Per Unit System .....	290
11.3	Three Phase Short Circuits.....	291
11.4	Reactance Diagrams.....	292
11.5	Percentage Values .....	292
11.6	Short Circuit kVA .....	293
11.7	Importance of Short Circuit Currents.....	294
11.8	Analysis of R-L Circuit.....	295
11.9	Three-Phase Short Circuit on Unloaded Synchronous Generator.....	296
11.10	Effect of Load Current or Prefault Current .....	299
11.11	Reactors.....	299
11.11.1	Construction of Reactors .....	300
11.11.2	Classification of Reactors .....	300
	<i>Worked Examples</i> .....	303
	<i>Problems</i> .....	329
	<i>Questions</i> .....	329

**CHAPTER 12: UNBALANCED FAULT ANALYSIS**

12.1	Sequence Impedances .....	331
12.2	Balanced Star Connected Load .....	331
12.3	Transmission Lines .....	333
12.4	Sequence Impedances of Transformer .....	334
12.5	Sequence Reactances of Synchronous Machine .....	335
12.6	Sequence Networks of Synchronous Machines .....	335
12.6.1	Positive Sequence Network .....	336
12.6.2	Negative Sequence Network.....	336
12.6.3	Zero Sequence Network.....	337

**(xii) Contents**

---

12.7	Unsymmetrical Faults .....	339
12.8	Assumptions for System Representation.....	339
12.9	Unsymmetrical Faults on an Unloaded Generator .....	339
12.10	Line-to-Line Fault .....	342
12.11	Double Line-to-Ground Fault.....	345
12.12	Single-Line-to-Ground Fault with Fault Impedance .....	348
12.13	Line-to-Line Fault with Fault Impedance .....	349
12.14	Double Line-to-Ground Fault with Fault Impedance.....	350
	<i>Worked Examples</i> .....	352
	<i>Problems</i> .....	365
	<i>Questions</i> .....	365

**CHAPTER 13: POWER SYSTEM STABILITY**

13.1	Elementary Concepts.....	367
13.2	Illustration of Steady State Stability Concept .....	368
13.3	Methods for Improving Steady State Stability Limit .....	369
13.4	Synchronizing Power Coefficient .....	369
13.5	Short Circuit Ratio and Excitation System.....	370
13.6	Transient Stability .....	371
13.7	Stability of a Single Machine Connected to Infinite Bus.....	371
13.8	The Swing Equation.....	372
13.9	Equal Area Criterion and Swing Equation .....	376
13.10	Transient Stability Limit .....	378
13.11	Frequency of Oscillations.....	379
13.12	Critical Clearing Time and Critical Clearing Angle .....	380
13.13	Fault on a Double-Circuit Line .....	383
13.14	Transient Stability when Power is Transmitted During the Fault.....	384
13.15	Fault Clearance and Reclosure in Double-Circuit System.....	385
13.16	First Swing Stability.....	386
13.17	Solution to Swing Equation Step-by-Step Method .....	386
13.18	Factors Affecting Transient Stability .....	389
	13.18.1 Effect of Voltage Regulator.....	390
13.19	Excitation System and the Stability Problem.....	391
13.20	Dynamic Stability .....	393
	13.20.1 Power System Stabilizer .....	394
13.21	Small Disturbance Analysis .....	394
13.22	Node Elimination Methods .....	397

13.23 Other Methods for Solution of Swing Equation.....	399
13.23.1 Modified Euler's Method.....	399
<i>Worked Examples</i> .....	401
<i>Problems</i> .....	420
<i>Questions</i> .....	420
<b>INDEX</b> .....	<b>421</b>